
#### The Ohm's Law

George Ohm has established experimentally in 1827 the following law


$$I = \frac{1}{R}V$$

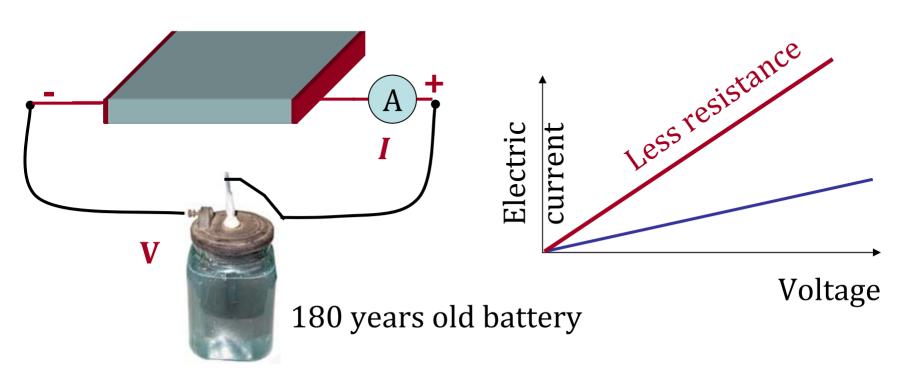V is the voltage across a conductor I is the current thought a conductor 1/R is a proportionality factor; R is called "resistance"




#### Ohm's Law

General type electric circuit:

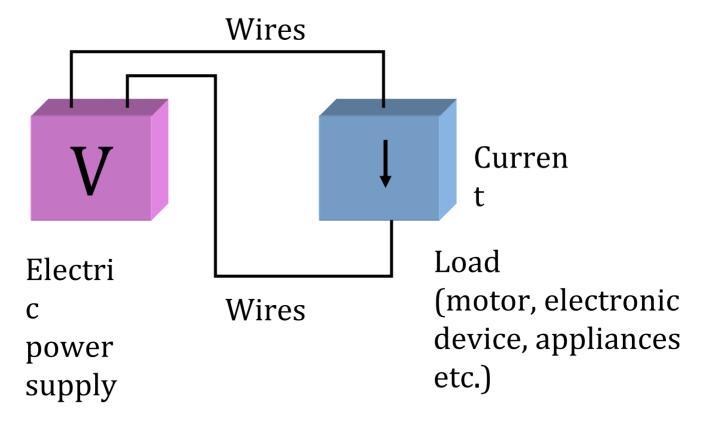


Given the power supply voltage V, how much current flows through the load?
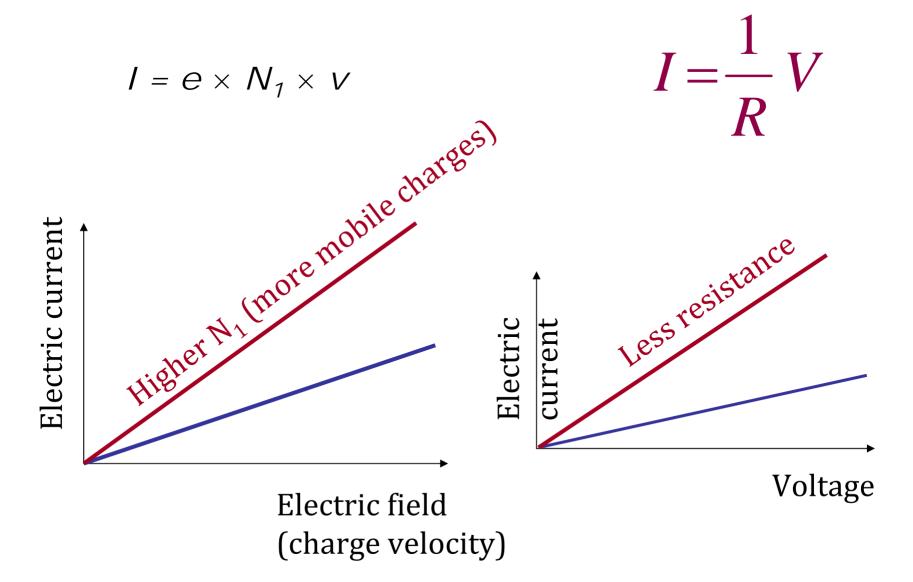
# Ohm's Law and electron charge transfer rate comparison


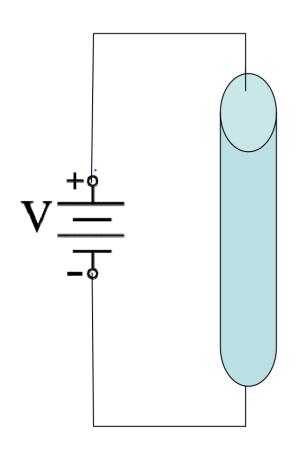
## **Experimental observations of Ohm's Law**



$$I = \frac{1}{R}V$$


Current


Voltage

Conductor length decreases

Current increases, i.e. R decreases
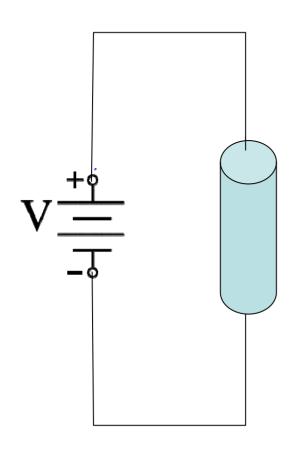
### **Experimental observations of Ohm's Law**



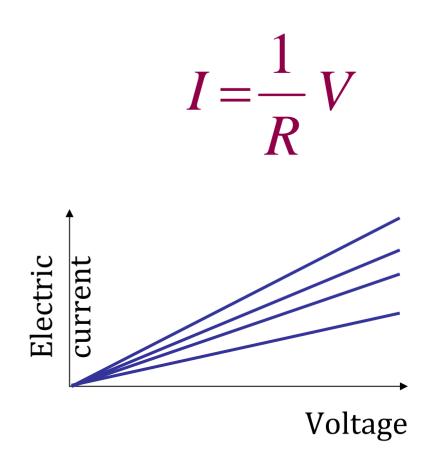

Conductor area increases

Current increases, i.e. R decreases

#### **Resistance and resistivity**

$$I = \frac{V}{R}$$

$$R = \rho \frac{L}{A}$$
L is the conductor length (along the current direction)
A is the cross-section area (with respect to the current direction)

 $\rho$  is called **resistivity** of the material;  $\rho$  does not depend on the conductor shape; it depends on mobile charge concentration and mobility in the material.

### Ohm's law, resistance and resistivity - summary

$$I = V/R$$

$$V = I \times R$$

Ohm's law in the form of I(V): the current through the conductor = applied voltage divided by the resistance Ohm's law in the form of I(V): the voltage needed to maintain the current I = current times resistance.

$$R = \rho \frac{L}{A}$$

A and L describe the geometry of the sample or wire.

The larger is the cross-section A the smaller is R, the higher is the current.

The longer is the wire length L, the higher is R, the smaller is the current;

$$R = \rho \frac{L}{A}$$

ρ describes the material ability to conduct the current.

The higher is  $\rho$ , the higher is R and the lower is the current

#### The units for resistance and resistivity

$$V = I \times R$$
  $R = \frac{V}{I}$ 

## Resistance R is measured in **Ohms** (**Ohm**, $\Omega$ )

1 Ohm is the resistance of the sample that passes the current of 1A when the voltage of 1 V is applied across it.

$$R = \rho \frac{L}{A} \qquad \qquad \rho = R \frac{A}{L} \left[ Ohm \frac{m^2}{m} = Ohm \cdot m \right]$$

Resistivity is measured in Ohm - meters (Ohm· m)

## Ohms' law using conductance and conductivity

Conductance

$$G=1/R$$

Using the conductance, the Ohm's law can be written as

$$I = \frac{1}{R} V = G \cdot V$$

Also, from 
$$G=1/R$$
 and  $R=\rho \frac{L}{A}$ ,  $G=1/R=\frac{1}{\rho} \frac{A}{L}$ 

$$\sigma = \frac{1}{\rho}$$
  $\sigma$  is called **conductivity** of the material (does not depend on the conductor shape)

Using conductivity, the conductance of the sample is given by

$$G = \sigma \frac{A}{L}$$

## **Ohm's Law using conductance - summary**

The expression that relates the electric current to the applied voltage

is called the Ohm's Law (established experimentally in 1827)

$$I = G \times V$$
, where

$$G = \sigma \frac{A}{L}$$
 is the conductance of the sample (wire),

 $\sigma$  is the conductivity of the material

A is the conductor cross-section area;

L is the conductor length along the current direction

#### The units for conductance and conductivity

$$I = G \times V$$
  $G = \frac{I}{V}$ 

## Conductance is measured in **Siemens (S)**

1 S is the conductance of the sample that passes the current of 1A when the voltage of 1 V is applied across it.

$$G = \sigma \frac{A}{L}$$

$$\sigma = G \frac{L}{A} \left[ S \frac{m}{m^2} = S/m \right]$$

Conductivity is measured in **Siemens per meter (S/m)** 

#### **Units and Dimensions**

Charge: Coulomb [C] abs (electron charge) **e** =

 $1.6 \times 10^{-19} \, \mathrm{C}$ 

Electric current: Ampere [A]

Electric voltage: Volt [V]


Resistance: Ohm [Ohm]

Resistivity [Ohm×m]

Conductance: Siemens [S]

Conductivity: [S/m, (Ohm×m)-1]

#### **Example 1: the Ohm's Law**

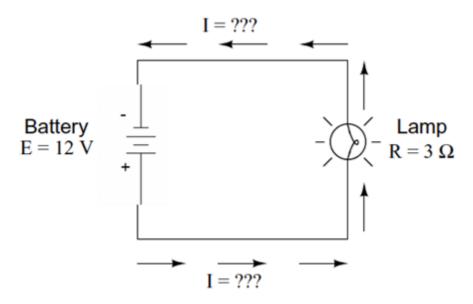

What is the amount of current (I) in this circuit?

$$V = I \times R$$

$$I = V / R$$

$$I = 12V / 3\Omega = 4A$$

Note: the notation for the battery voltage is usually "V" or "E"

### Resistivity of different materials

**Wires** are used to connect different components in the network; Wires have very low resistance



**Resistors** are used to dissipate the power and to change the voltage (potential).

(potential):	
Material	Electric Resistivity (×10 <sup>-9</sup> Ohm·m)
Aluminum [Al]	27
Aluminum Alloy	50
Brass	20 - 61
Carbon [C]	1.4 × 10 <sup>4</sup>
Copper [Cu]	17
Copper Alloy	17 - 490
Gold [Au]	24
Iron [Fe]	97

### Example 2

Find the resistance of a **wire** made of **copper** [Cu] ( $\rho = 17*10^{-9}$  Ohm-m). The wire is 1 m long and is 1 mm in diameter.

$$R = \rho * L/A$$

$$L = 1 \text{ m}; D = 1 \text{mm} = 10^{-3} \text{ m};$$

The area, 
$$A = \pi^*D^2/4 = 3.14^*(10^{-3})^2/4 = 7.85^*10^{-7} \text{ m}^2$$

The resistance

$$R = 17*10^{-9} \text{ Ohm*m*1m} / 7.85*10^{-7} \text{ m}^2 = 2.17*10^{-2} \text{ Ohm} = 21.7 \text{ mOhm}$$

What voltage across this wire is required to have the 100 mA current through it?

$$V = I \times R = 100 \text{ e}-3 \times 21.7 \text{e}-3 = 0.00217 \text{ V}$$

### **Example 3**

Find the resistance of a **carbon resistor**, which is 1 cm long and 0.1 mm in diameter

R = 
$$\rho$$
 \*L/A;  $\rho$  = 1.4 × 10<sup>4</sup> \* 10<sup>-9</sup> Ohm\*m = 1.4 × 10<sup>-5</sup> Ohm\*m;  
L = 1 cm = 10<sup>-2</sup>m; A = 7.85\*10<sup>-9</sup> m<sup>2</sup>

 $R = 1.4*10^{-5} \text{ Ohm*m*}10^{-2} \text{ m} / 7.85*10^{-9} \text{ m}^2 = 17.8 \text{ Ohm}$ 

**Compare**: Cu – wire,  $R_1 = 21.7 \text{ mOhm} \approx 0.02 \text{ Ohm}$ ;

Carbon-resistor,  $R_2 = 17.8 \text{ Ohm} \approx 18 \text{ Ohm}$ ;

To have the current through the Cu-wire of 0.1 A, the required voltage across the wire,  $V_1 = I*R_1 = 0.002 \text{ V}$ ;

To have the same current through the Carbon-resistor, the required voltage across the resistor is  $V_2 = I*R_2 = 1.8 \text{ V}$ ;