
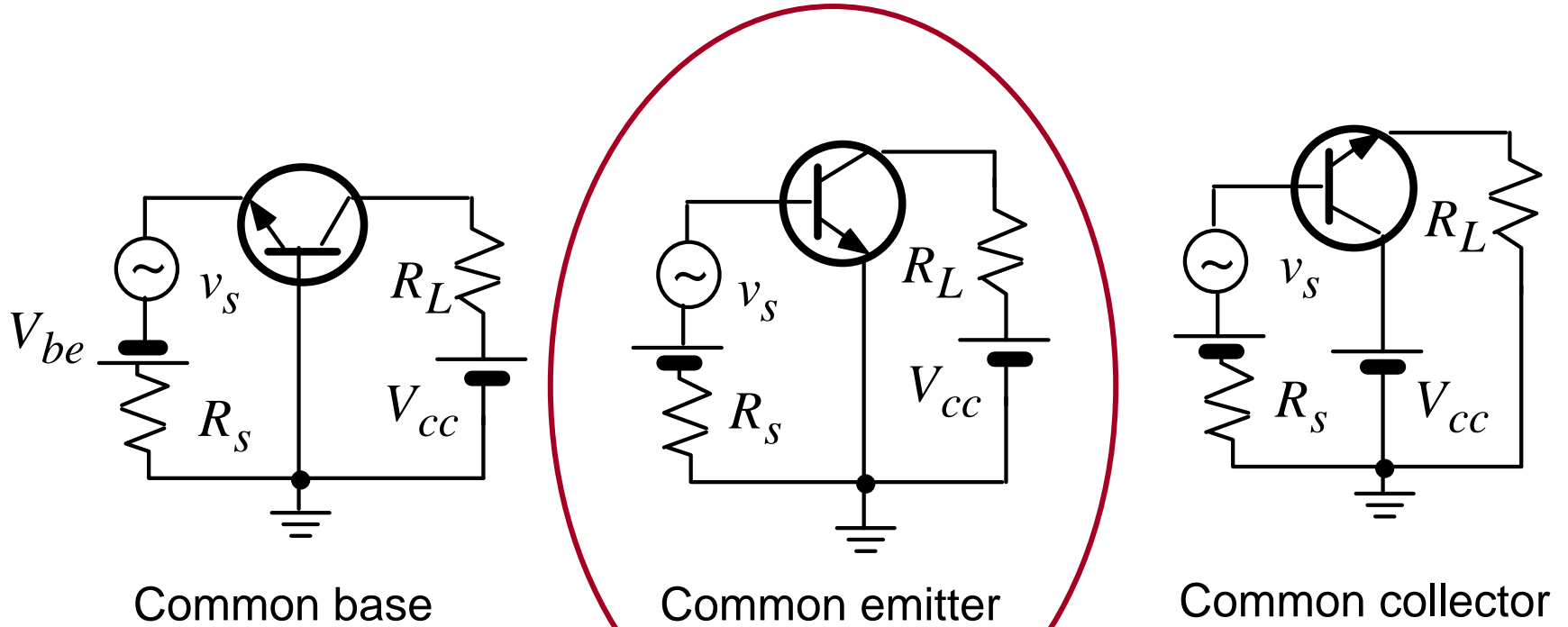



# BJT Circuit Configurations

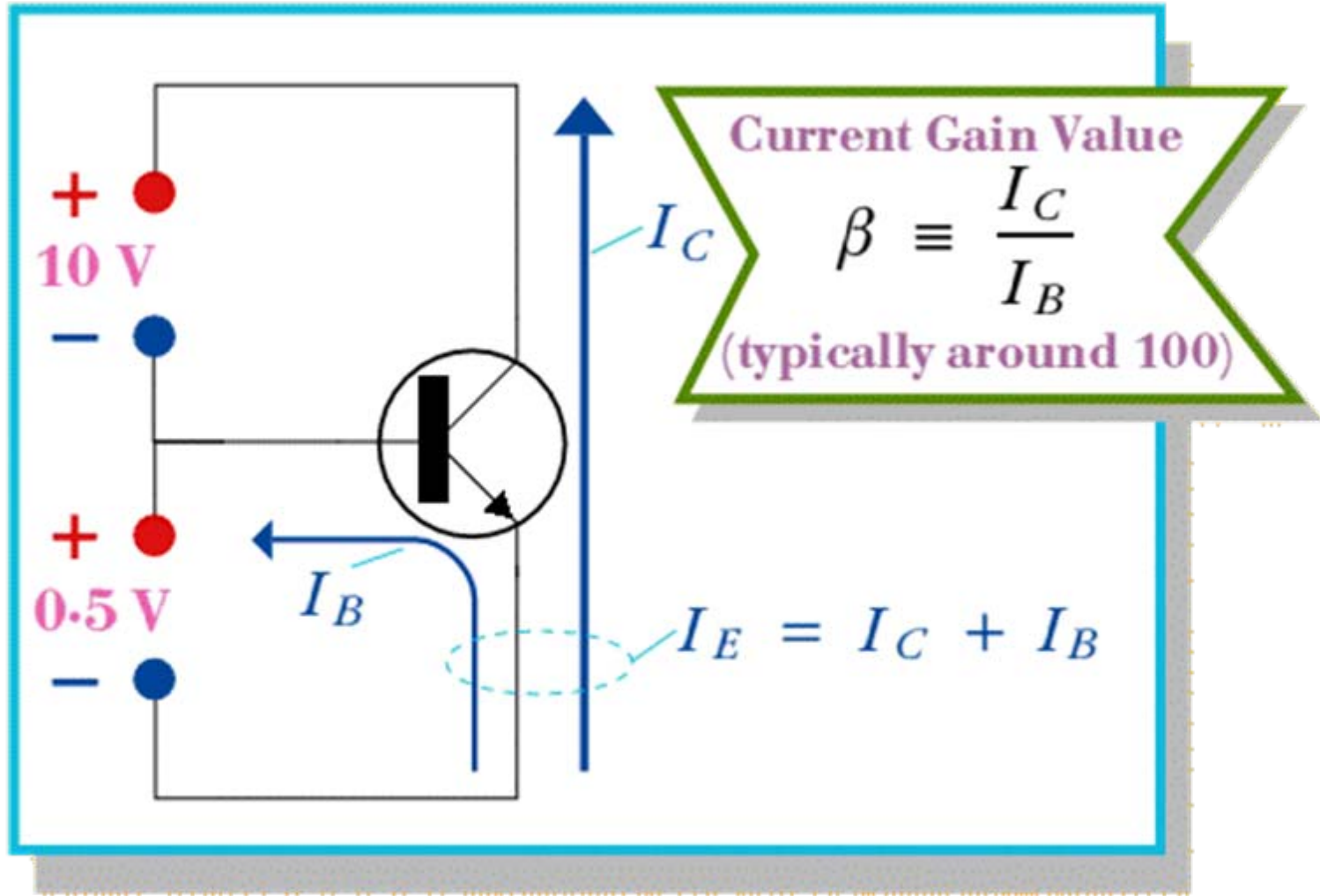

# Common emitter current gain





# BJT Current-Voltage Characteristics

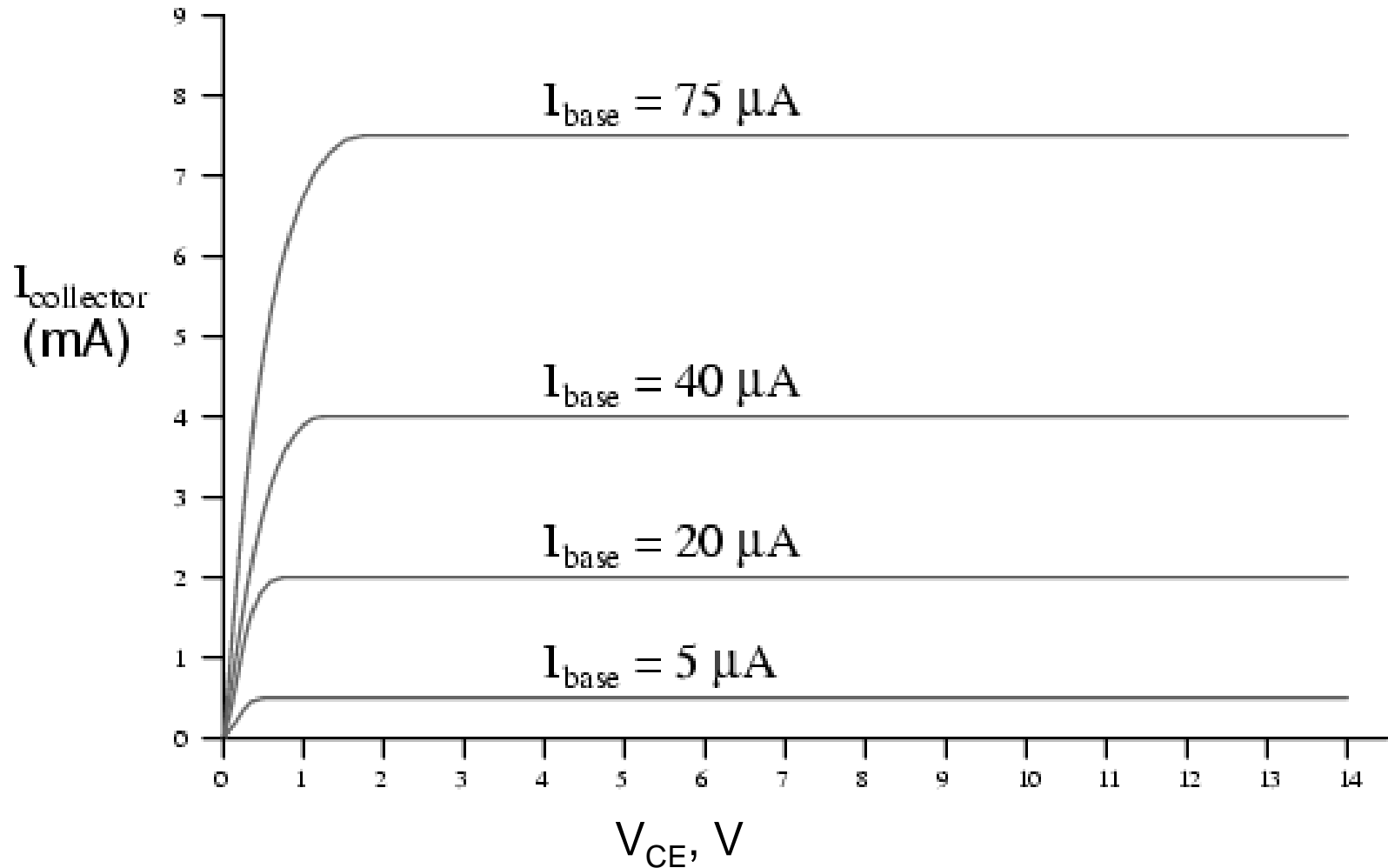

**Very small base current ( $\sim 5\text{-}75 \mu\text{A}$ )  
causes much higher collector current (up to 7.5 mA).  
The current gain is  $\sim 100$**
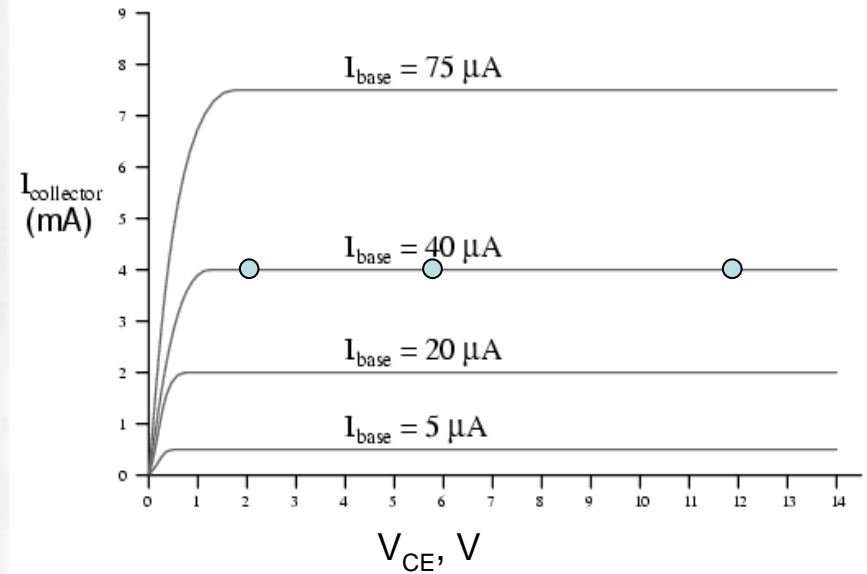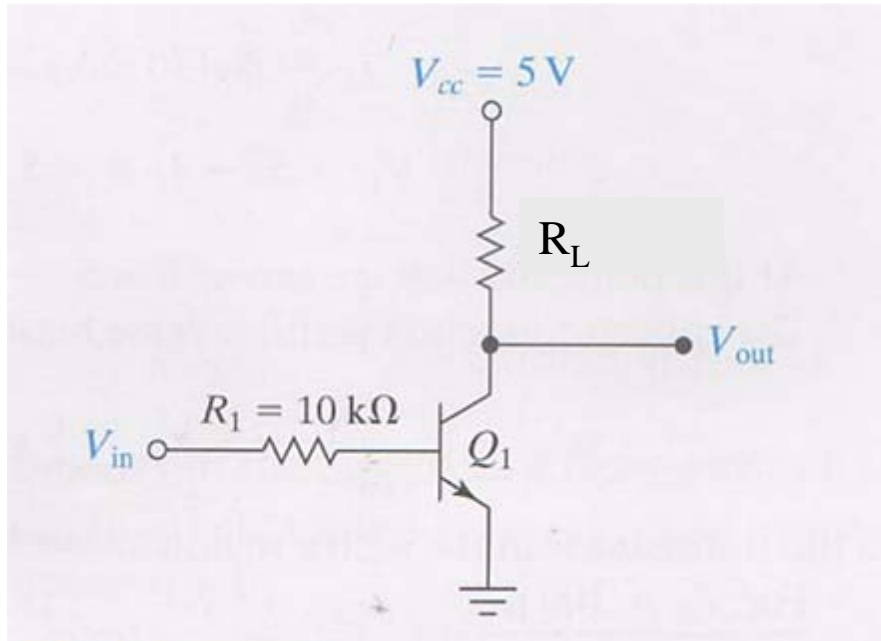
## BJT amplifier circuit analysis: Operating point





Collector current depends on two circuit parameters:  
the base current and the collector voltage.

At high collector voltage the collector current depends on the base current only.

For  $I_{base} = 40\text{ }\mu\text{A}$ ,  $I_{coll} = 4\text{ mA}$  for any  $E_{C-E}$  greater than 1.5 V
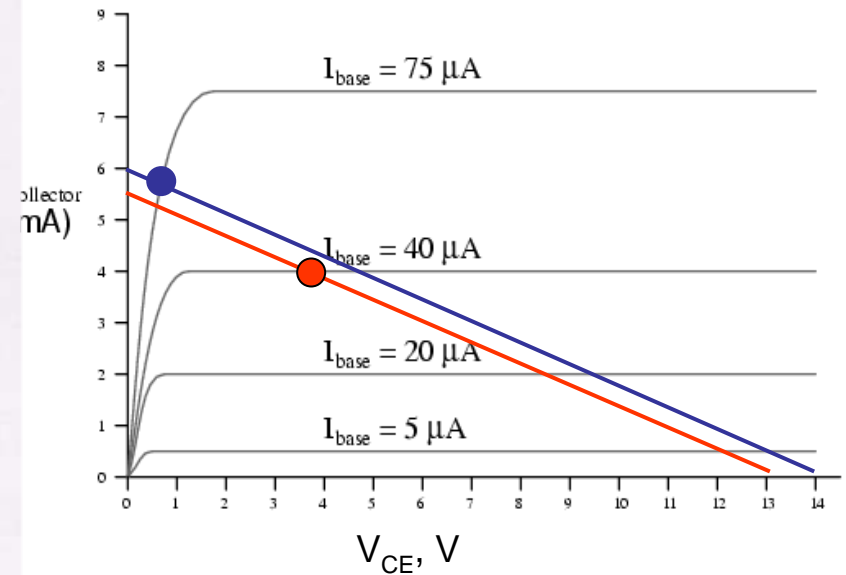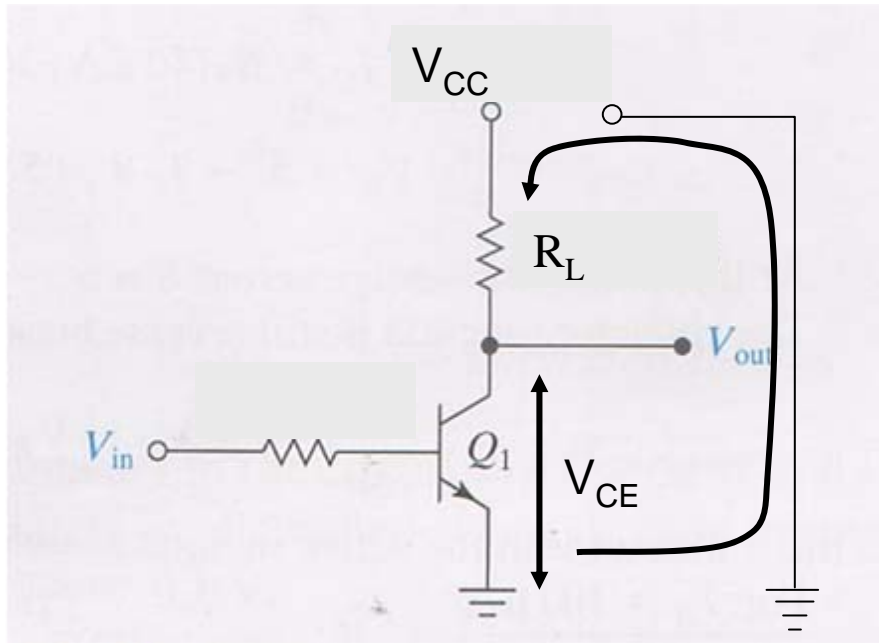
## BJT amplifier circuit analysis: Operating point



For an arbitrary collector voltage, collector current can be found using the KVL.

The KVL for the collector – emitter circuit,  $V_{CC} = I_{RL} \times R_L + V_{CE}$ ;


$$I_{RL} = \frac{V_{CC} - V_{CE}}{R_L} \quad \text{The } R_L \text{ current depends linearly on the collector voltage } V_{CE}$$

Resistor  $R_L$  and the C-E circuit of BJT are connected in series, hence  $I_{RL} = I_C$

For  $I_b = 40 \mu\text{A}$  and  $V_{CC} = 13\text{V}$ , the collector current  $I_C = 4 \text{ mA}$


For  $I_b = 75 \mu\text{A}$  and  $V_{CC} = 14\text{V}$ , the collector current  $I_C = 4 \text{ mA}$

## BJT amplifier gain analysis: 1

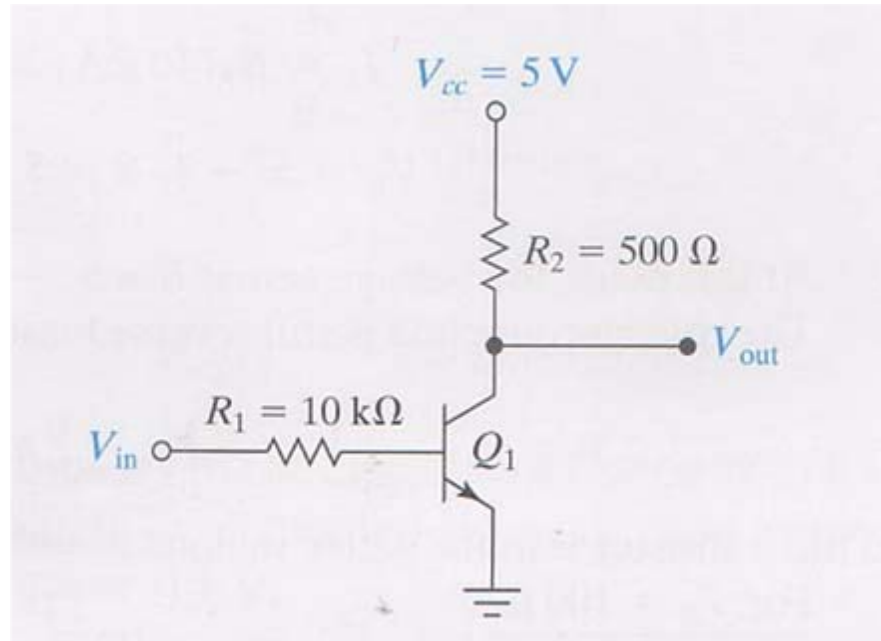


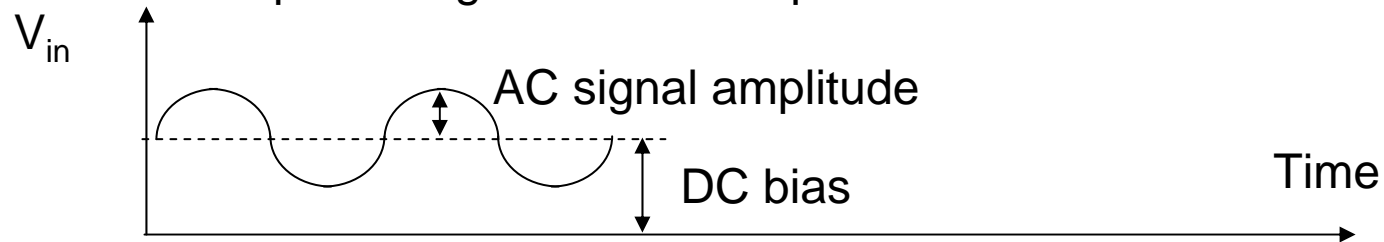
### 1. Input circuit

The input voltage has two components: the DC bias and the AC signal




DC voltage component biases the base-emitter p-n junction in the forward direction  
AC component is the input signal to be amplified by the BJT.

## BJT amplifier gain analysis: 2

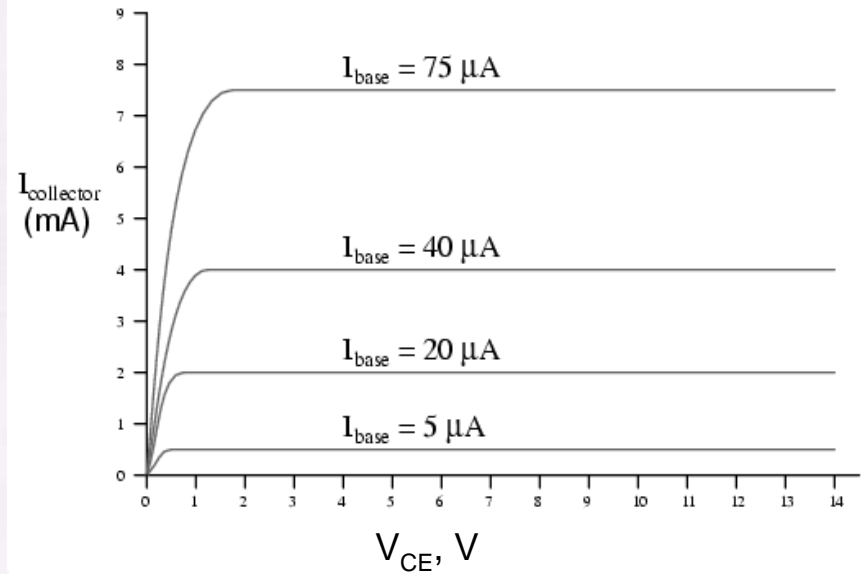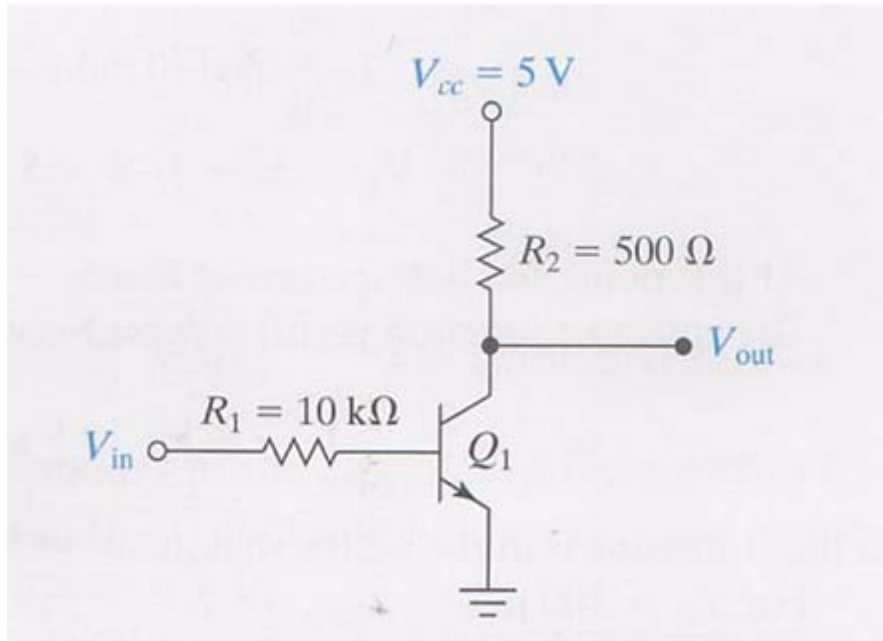


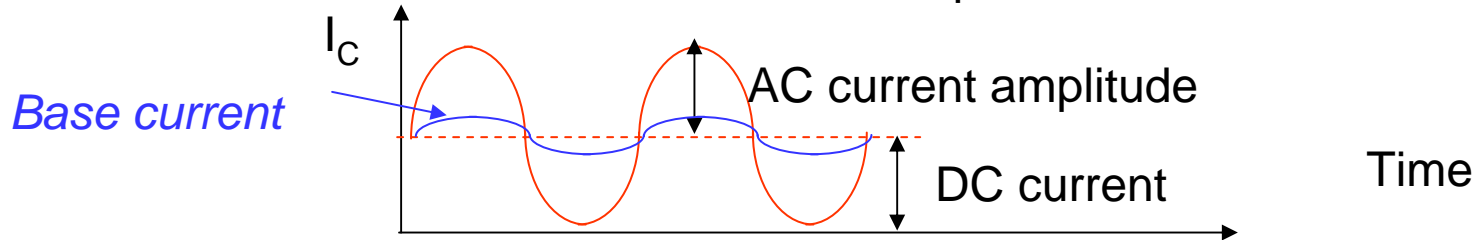
### 2. Output circuit

The collector current has two components too.



DC and AC collector currents flow through the BJT in accordance with its I-V characteristics

## BJT amplifier gain analysis: 3

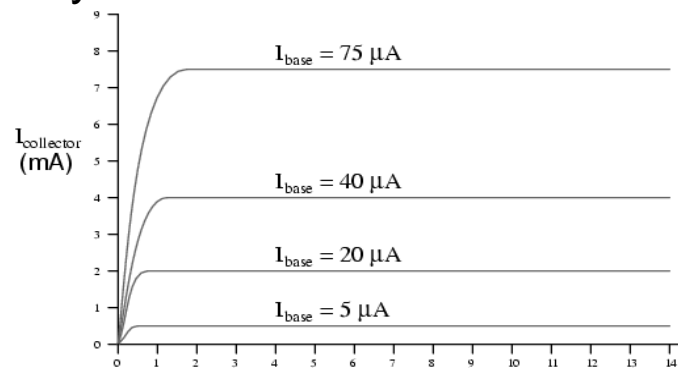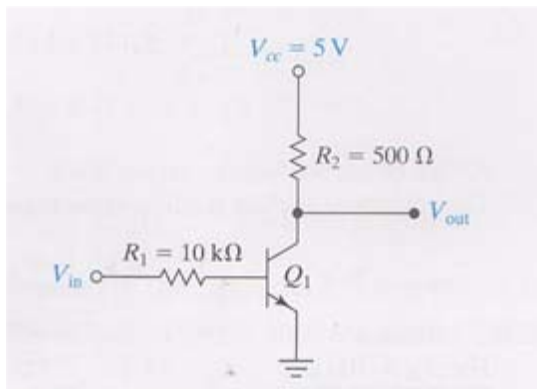

The resistance of the B-E junction is very low when  $V_{BE} \geq V_{BE0} \approx V_{bi} \approx 0.7 \text{ V}$ .

Hence the base current  $I_B \cong (V_{in} - V_{BE0})/R_1 = (V_{inDC} - V_{BE0} + V_{inAC})/R_1$

The collector current  $I_C$  does not depend on the collector voltage if the latter is high enough.

Hence,  $I_C \cong \beta I_B$ ;

The voltage drop across the load resistance  $R_2$ :  $V_2 = I_C R_2$ ;

The output voltage  $V_{out} = V_{CC} - V_2 = V_{CC} - I_C R_2$ ;

$V_{out} = V_{CC} - I_C R_2 = V_{CC} - \beta I_B R_2 = V_{CC} - \beta R_2 (V_{inDC} - V_{BE0} + V_{inAC})/R_1$ ;



In signal amplifiers only AC component of the output voltage is important:

$$V_{outAC} = -\beta R_2 V_{inAC}/R_1;$$

The amplifier voltage gain:  $k_V = V_{outAC}/V_{inAC} = -\beta R_2/R_1$ ;



## BJT amplifier gain analysis: 4

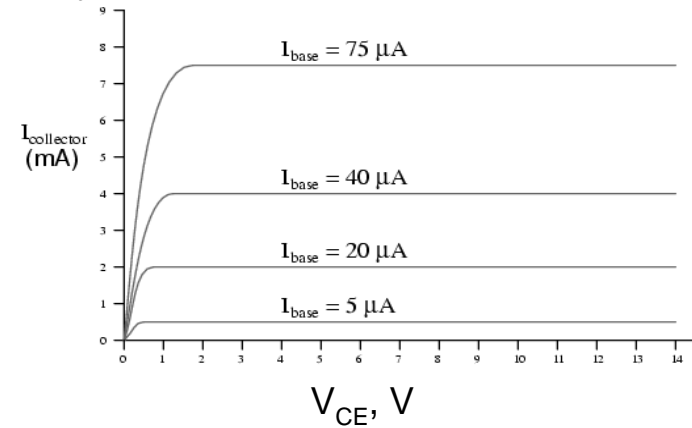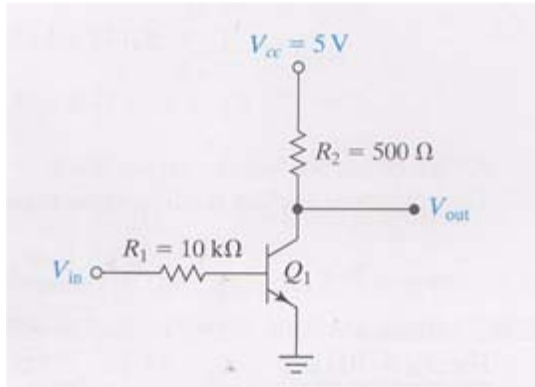


### Common emitter gain summary:

Current gain:  $k_I = \beta$


Voltage gain:  $k_V = V_{outAC}/V_{inAC} = -\beta R_2/R_1$ ;

Power gain:  $k_P = k_V \times k_I = -\beta^2 \times R_2/R_1$
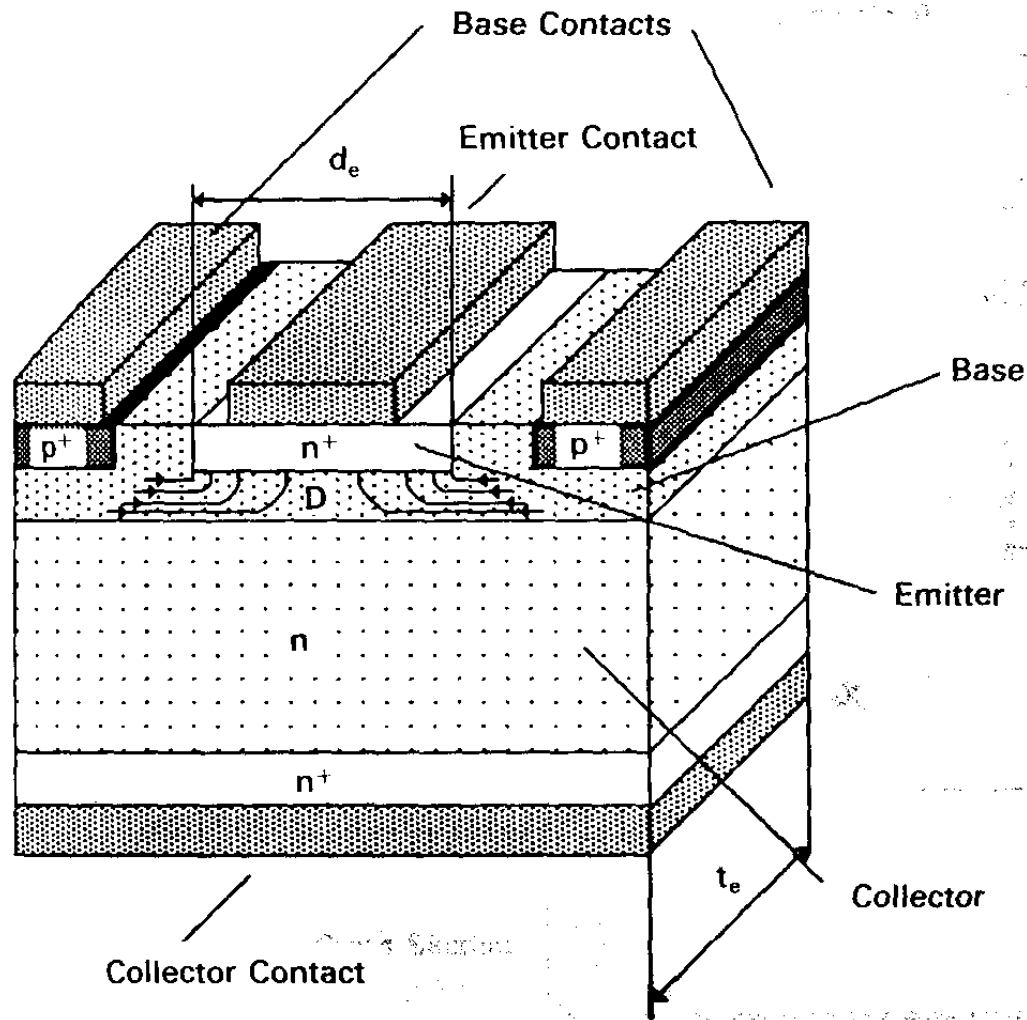
# BJT design and factors affecting the performance


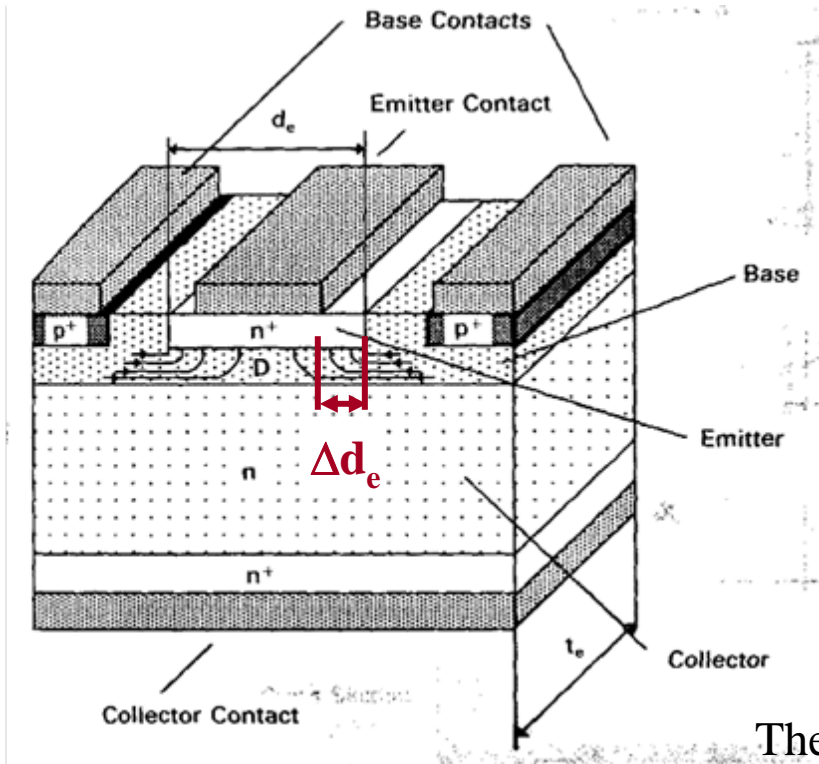
# Base resistance and emitter current crowding in BJTs



The voltage drop along the base layer  $V_{bb} = r_{bb} I_b$ , where  $r_{bb}$  is called the base spreading resistance.


The p-n junction current decreases rapidly when the voltage drops by  $\Delta V_{bb} \sim V_{th} = kT/q$

$$I = I_s \left( e^{\frac{qV}{kT}} - 1 \right) = I_s \left( e^{\frac{V}{V_{TH}}} - 1 \right)$$

The length of the edge region,  $\Delta d_e$ , where most of the emitter current flows may be estimated from:

$$V_{th} = I_b R_{b_{max}} \approx I_b \rho_b \frac{\Delta d_e}{t_e W}$$
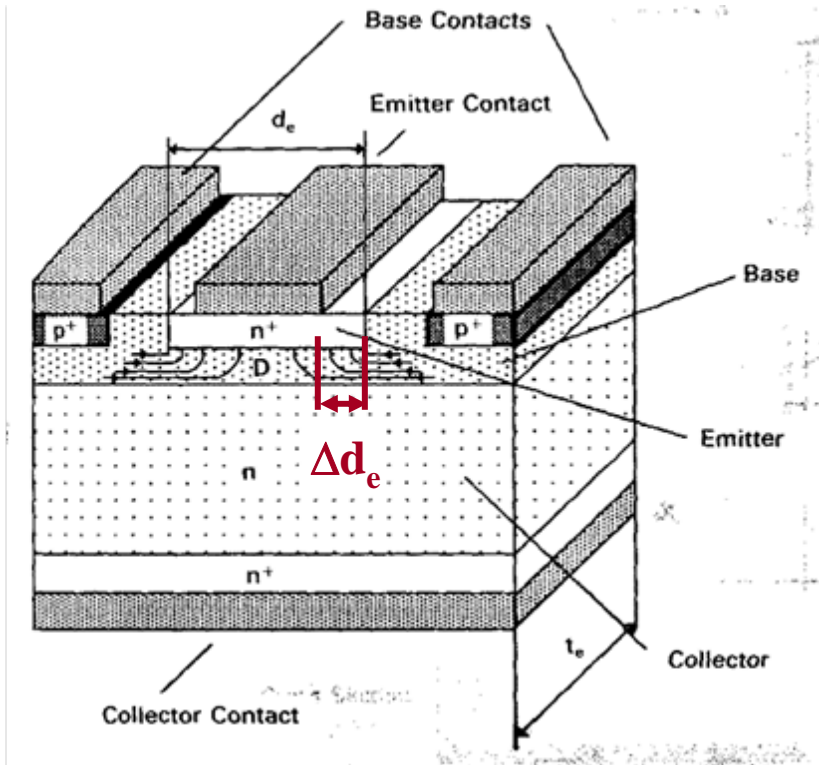
## Emitter current crowding in BJTs (cont.)




$$V_{th} = I_b R_{b\max} \approx I_b \rho_b \frac{\Delta d_e}{t_e W}$$

$$\rho_b = \frac{1}{q N_b \mu_b}$$

From these,

$$\Delta d_e \approx \frac{V_{th} t_e W}{I_b \rho_b} = \frac{V_{th}}{I_b} q N_b \mu_b t_e W_b$$

## Example

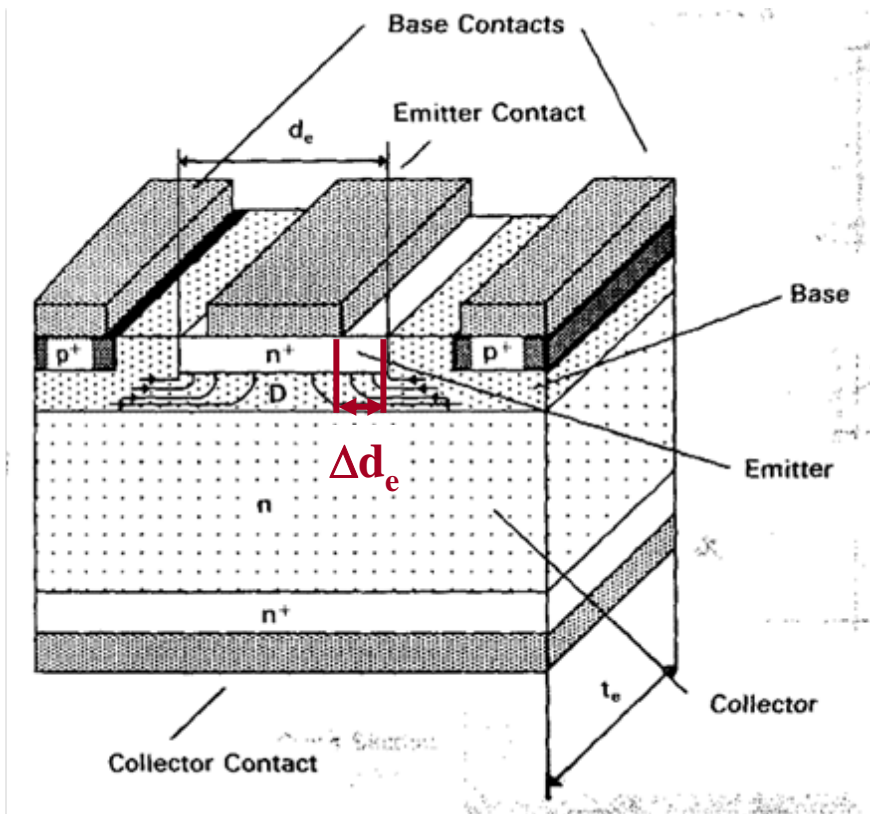

Estimate the effective emitter length,  $\Delta d_e$  for the BJT having the following parameters:

$$I_b = 50 \mu\text{A};$$

$$N_b = 10^{17} \text{ cm}^{-3}$$

$$\mu_b = 400 \text{ cm}^2/\text{V}\cdot\text{s}$$



$$W_b = 0.1 \mu\text{m}$$

$$t_e = 100 \mu\text{m}$$

$$\Delta d_e \approx \frac{V_{th}}{I_b} q N_b \mu_b t_e W_b$$


$$\Delta d_e = 3.33 \text{ e-4 cm} = 3.33 \mu\text{m}$$

# Large periphery BJT Design

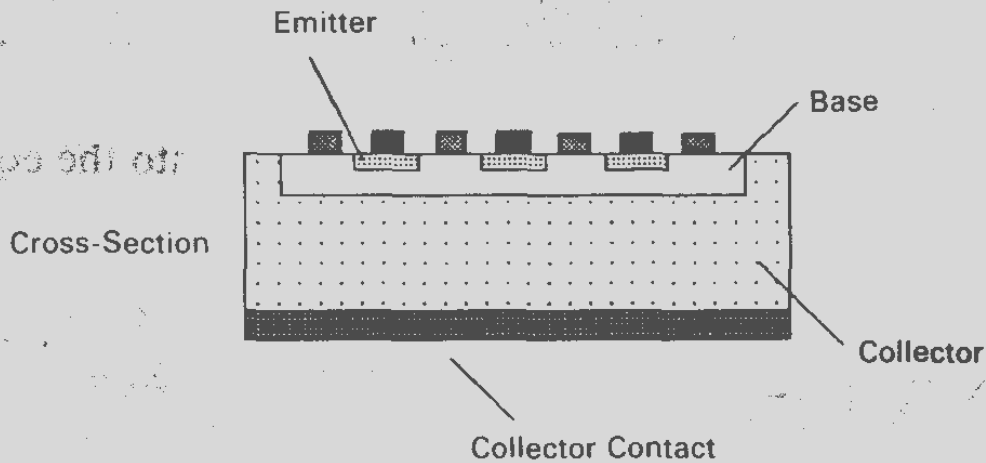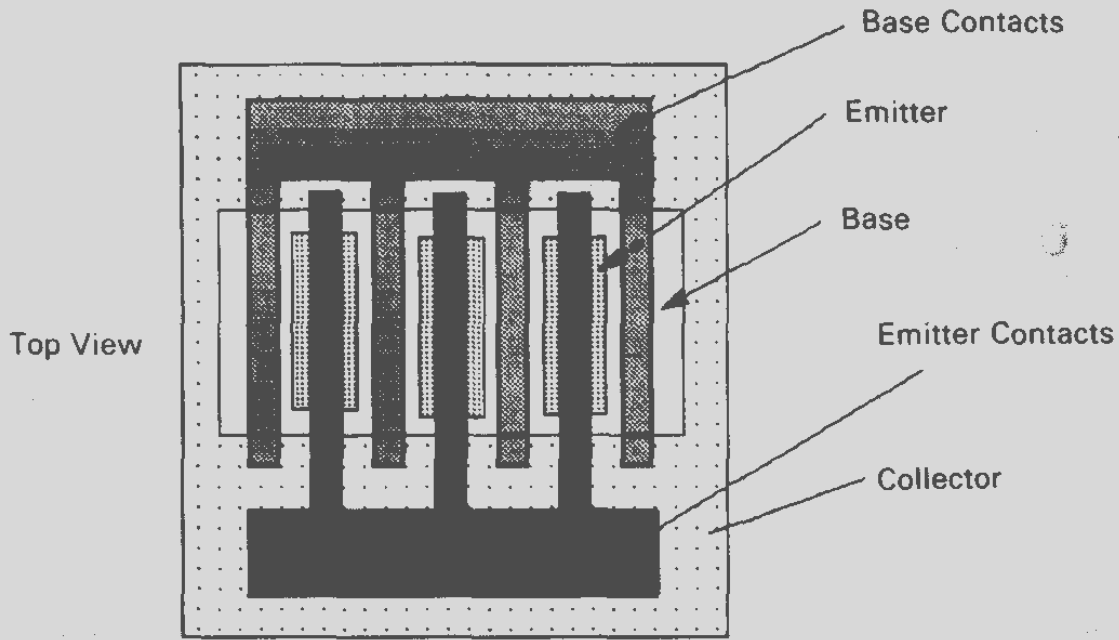
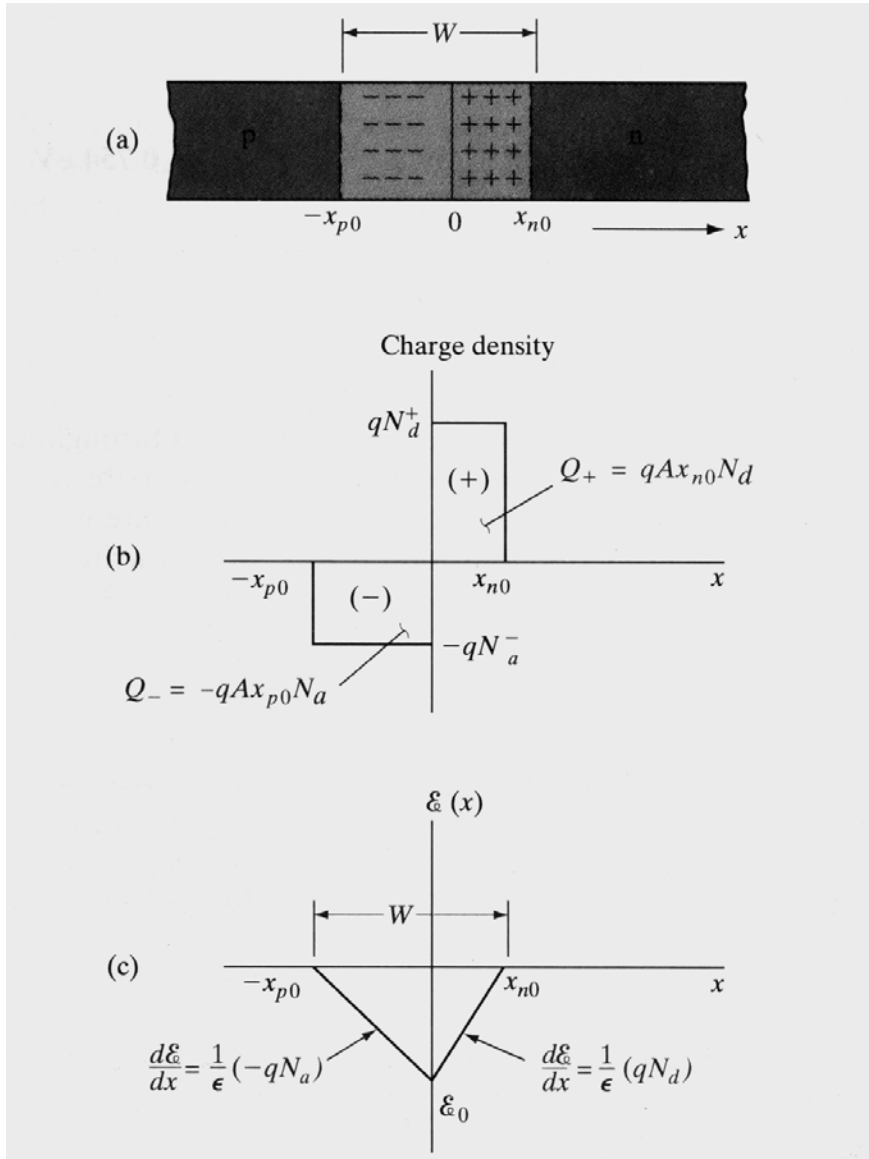
# Base narrowing (Early effect)

The depletion width of the p-n junction depends on the applied voltage:



(Here  $W$  is the depletion region width not the width of the base as in BJT!)

In the BJT, this effect means that the effective width of the base is less than  $W_b$ :

$$W_{eff} = W_b - X_{deb} - X_{dcb}$$

where  $W_b$  is the physical thickness of the base,

$x_{deb}$  and  $x_{dcb}$  are the depletion region widths from the emitter and collector sides.

The depletion widths are given by ( $N_e \gg N_b$ ):

$$x_{deb} = \left[ \frac{2\epsilon\epsilon_0 (V_{bi} - V_{be})}{q N_b} \right]^{1/2}$$

$$x_{dcb} = \left[ \frac{2\epsilon\epsilon_0 (V_{bi} + V_{cb}) N_c}{q N_b^2} \right]^{1/2}$$

$x_{dcb}$  is usually the most important factor since the voltage applied to collector is high.

The doping level in collector,  $N_{DC}$  has to be lower than that of the base,  $N_{AB}$ , to reduce the Early effect:


$$N_C \ll N_B$$



Due to Early effect the effective base thickness depends on the collector voltage.



In the gain expression,  $W$  should be replaced with  $W_{\text{eff}}$ :
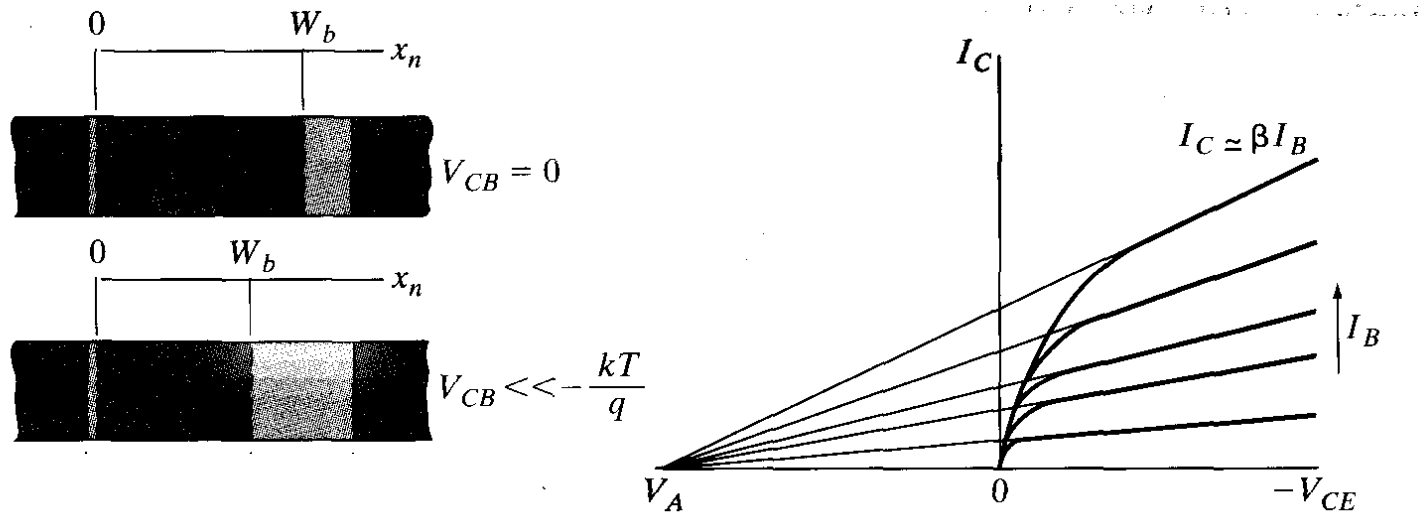
$$\beta_{\text{rec}} = \frac{2L_p^2}{W_{\text{eff}}^2}$$



The Early effect decreases the output resistance, and hence the voltage gain of BJTs.
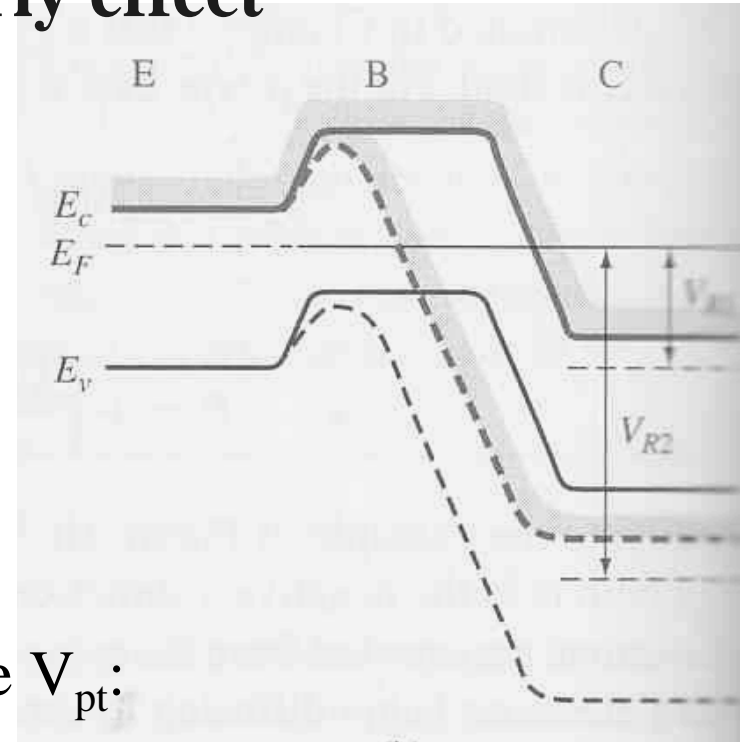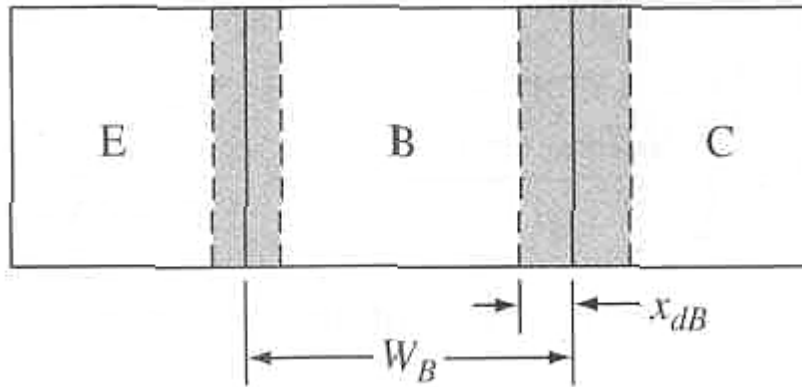
# Punch-through breakdown in BJTs - - the result of the Early effect




The punch-through breakdown voltage  $V_{pt}$ :

$$W = x_{dcb}$$

$$V_{pt} = \frac{qW^2}{2\epsilon\epsilon_0} \frac{N_b(N_c + N_b)}{N_c}$$
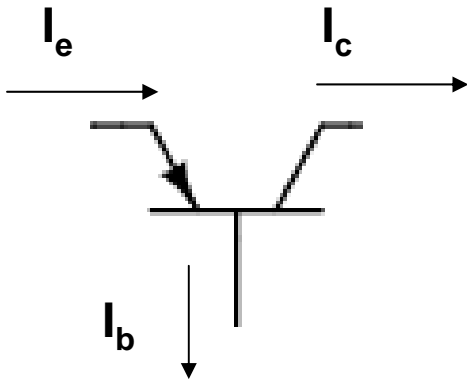
# BJT Model

- Gummel-Poon model used in SPICE and other simulators**



Applying KCL to the BJT terminals:

$$I_e = I_c + I_b$$

Collector – emitter current relationship:

$$I_c = \alpha I_e$$

where  $\alpha$  is called a common base current gain

Hence,

$$I_c = \alpha (I_c + I_b)$$

$$I_c = \frac{\alpha}{1 - \alpha} I_b$$

$$I_c = \beta I_b$$


$$\beta = \frac{\alpha}{1 - \alpha}$$

$$\alpha = \frac{\beta}{1 + \beta}$$

Common emitter current gain is defined as:

The last two expressions link common emitter and common base current gains
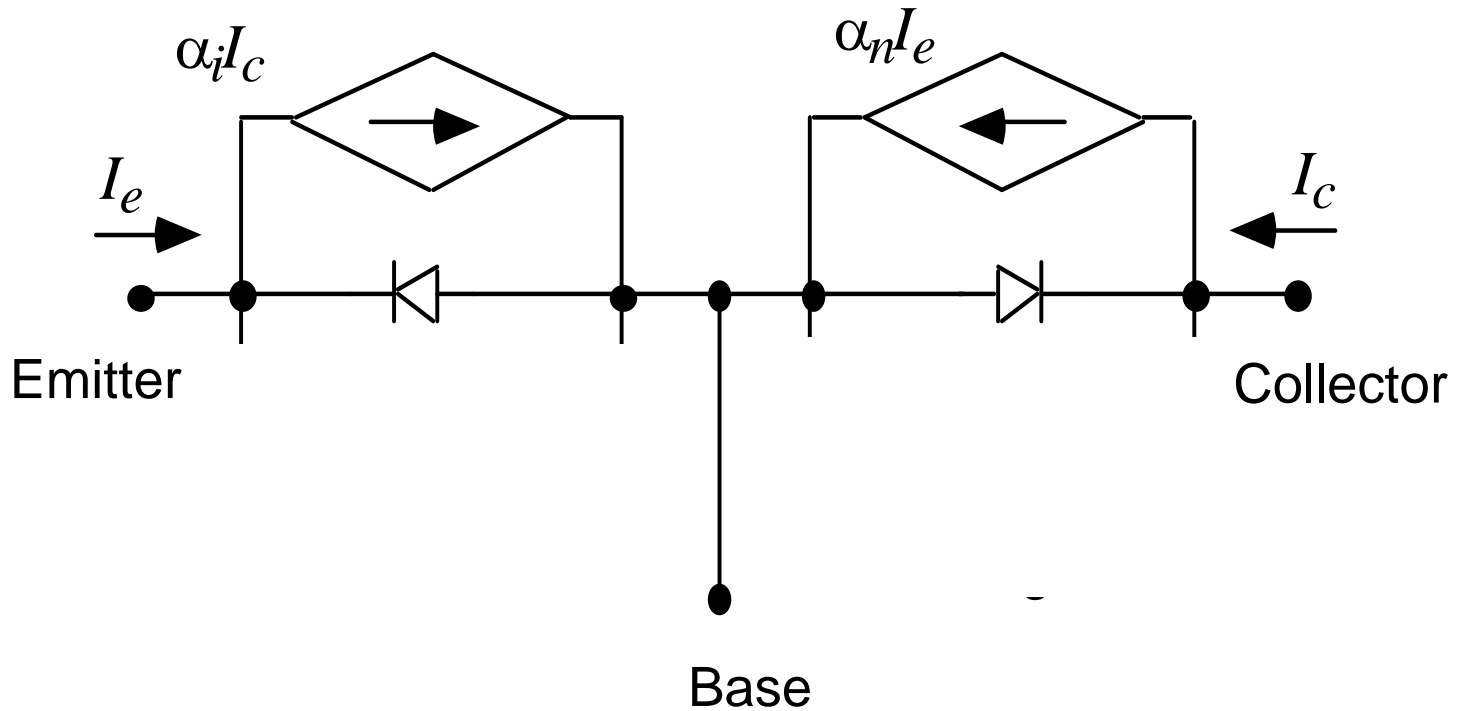
# Simplified Gummel-Poon BJT equivalent circuit



- Emitter junction:


$$I_{be} = \frac{I_{se}}{\beta_F} \left[ \exp\left(\frac{V_{be}}{n_F V_{th}}\right) - 1 \right]$$

- Collector junction:

$$I_{bc} = \frac{I_{sc}}{\beta_R} \left[ \exp\left(\frac{V_{bc}}{n_R V_{th}}\right) - 1 \right]$$

$$V_{th} = kT/q = 0.026 \text{ V at } 300 \text{ K}$$
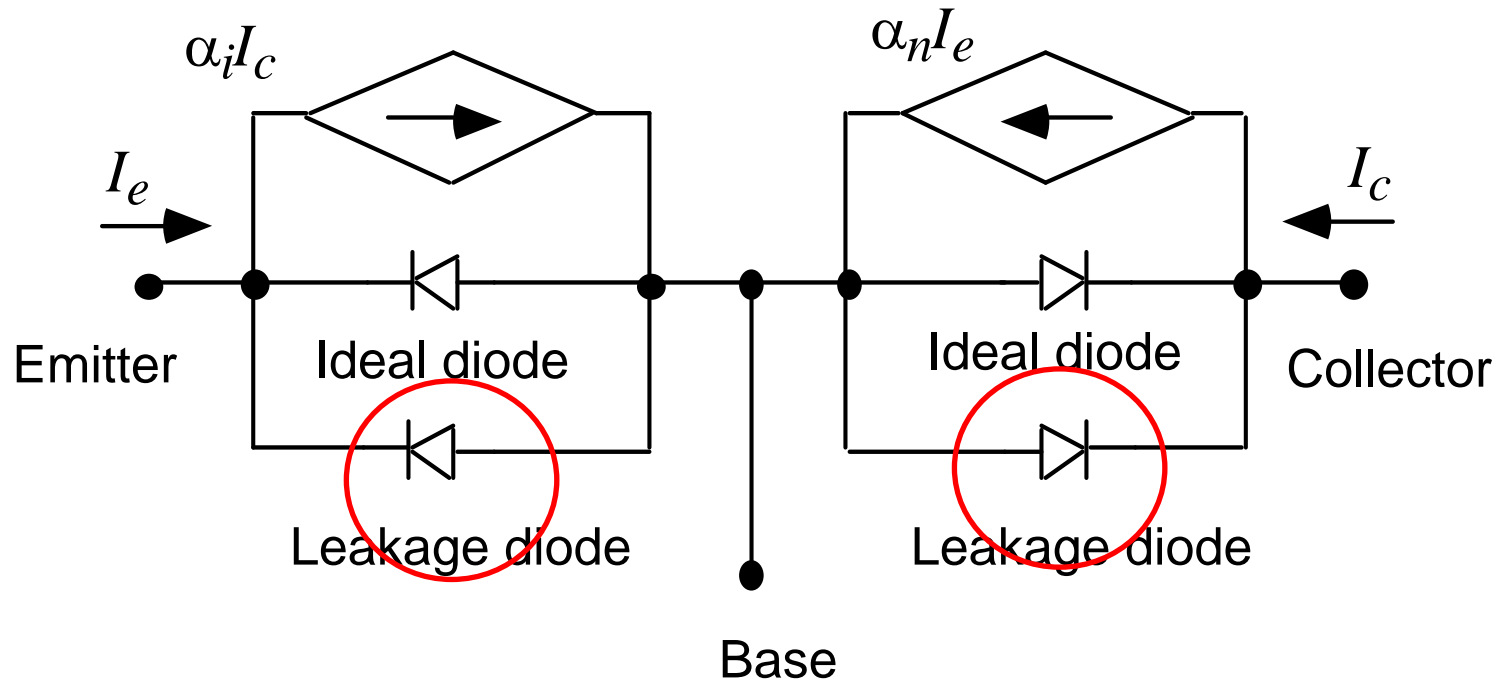
# Gummel-Poon BJT equivalent circuit accounting for the leakage currents



• Emitter –base leakage

diode:

$$I_{Leak\_be} = I_{se} \left[ \exp\left(\frac{V_{be}}{n_E V_{th}}\right) - 1 \right]$$

Collector –base leakage diode:

$$I_{Leak\_bc} = I_{sc} \left[ \exp\left(\frac{V_{bc}}{n_C V_{th}}\right) - 1 \right]$$