
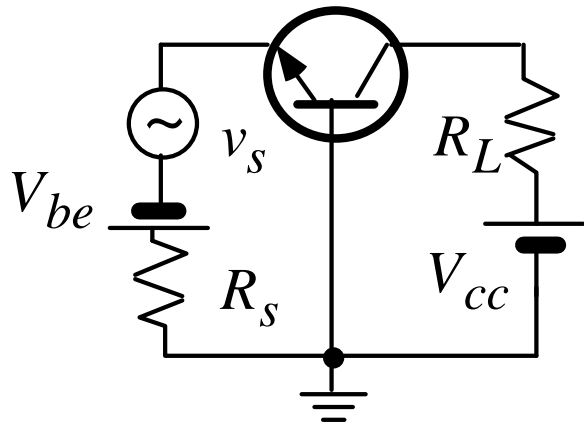



BJT Circuit Configurations

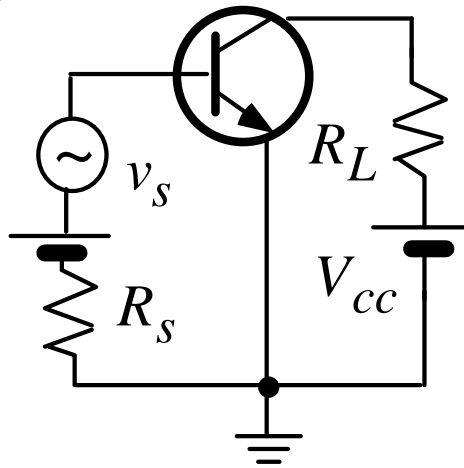

Common base




Common emitter

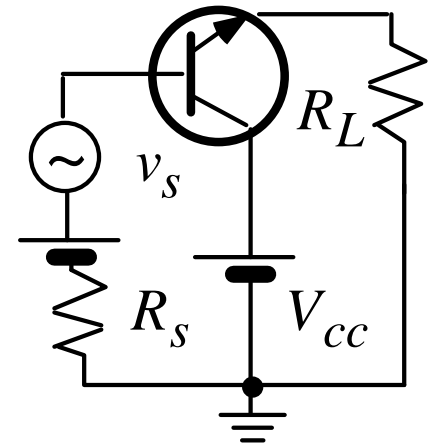


Common collector

Common emitter current gain


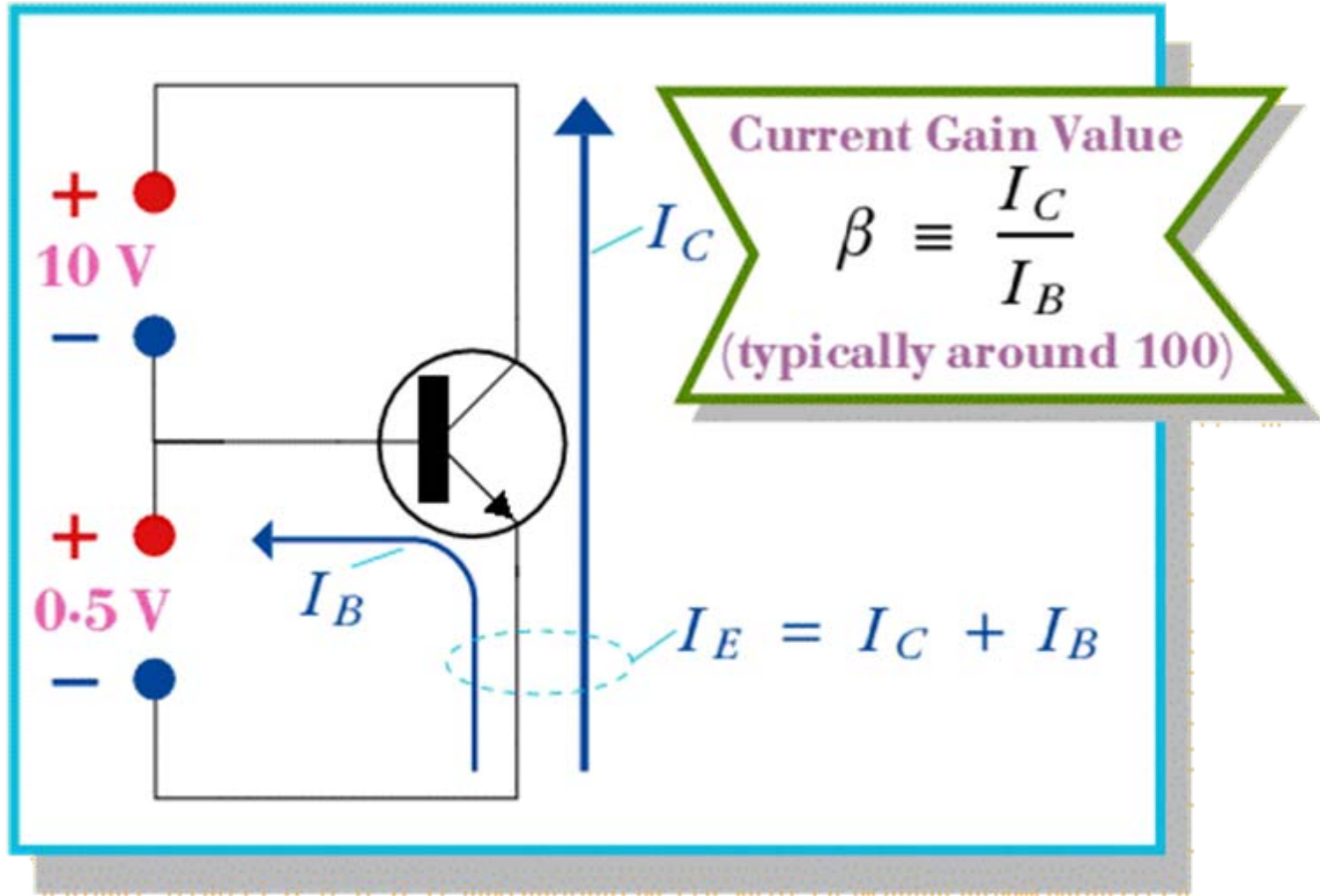


BJT Current-Voltage Characteristics

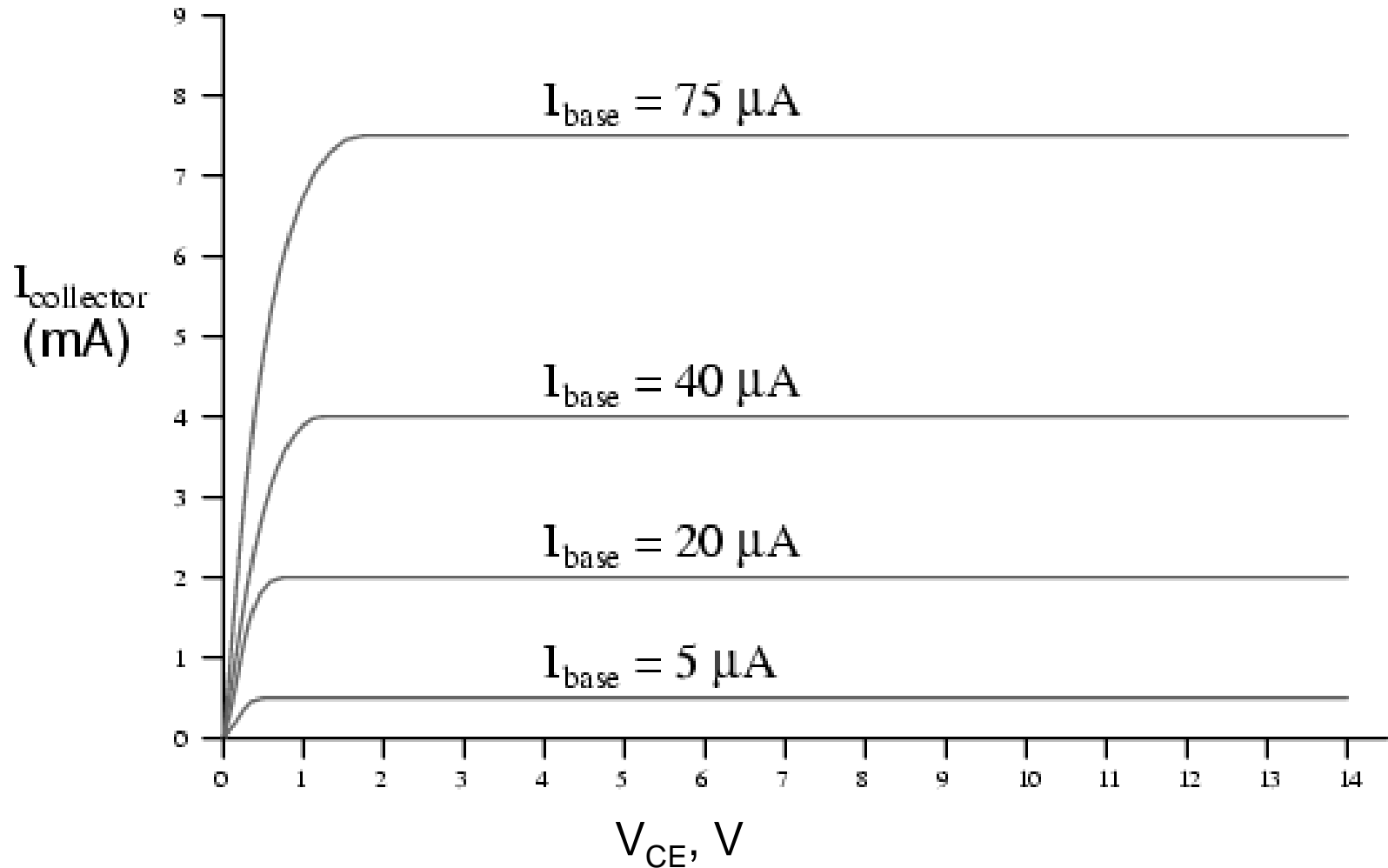

**Very small base current ($\sim 5\text{-}75 \mu\text{A}$)
causes much higher collector current (up to 7.5 mA).
The current gain is ~ 100**

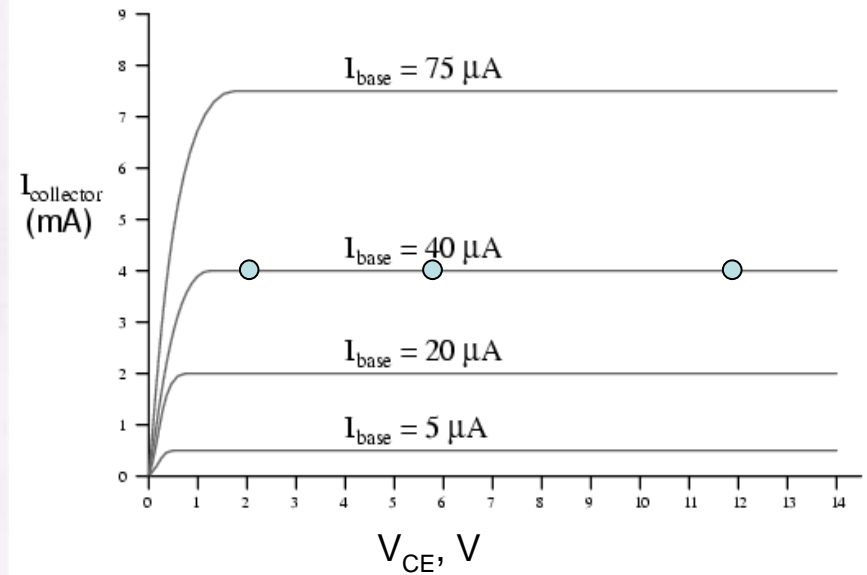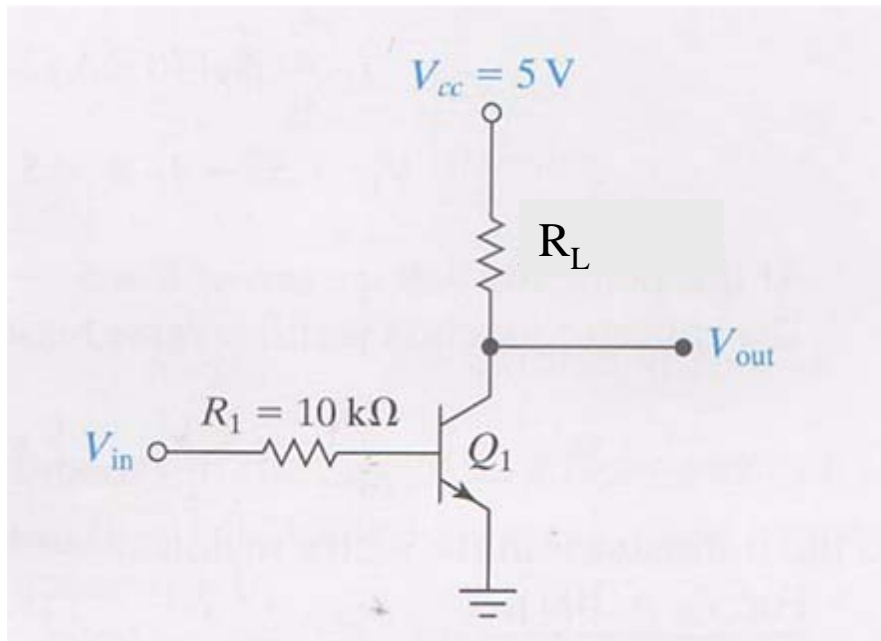BJT amplifier circuit analysis: Operating point





Collector current depends on two circuit parameters:
the base current and the collector voltage.

At high collector voltage the collector current depends on the base current only.

For $I_{base} = 40\text{ }\mu\text{A}$, $I_{coll} = 4\text{ mA}$ for any E_{C-E} greater than 1.5 V

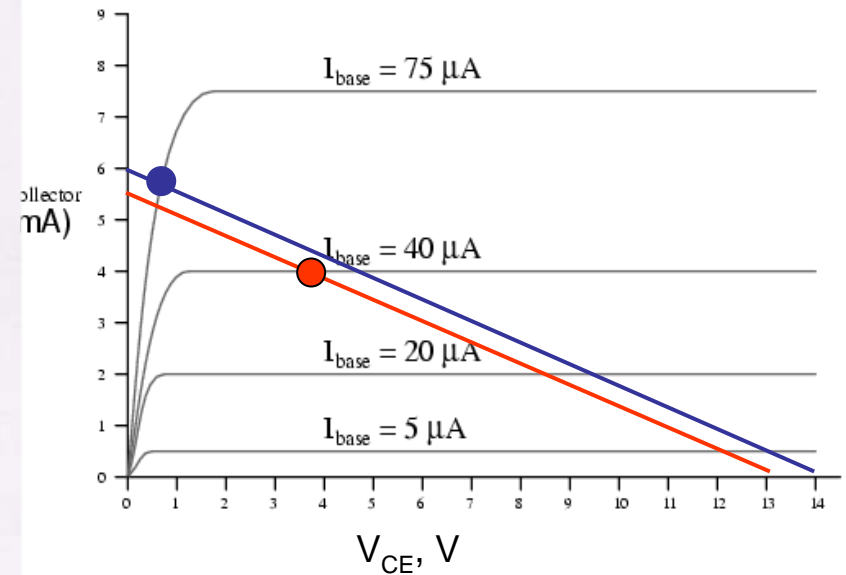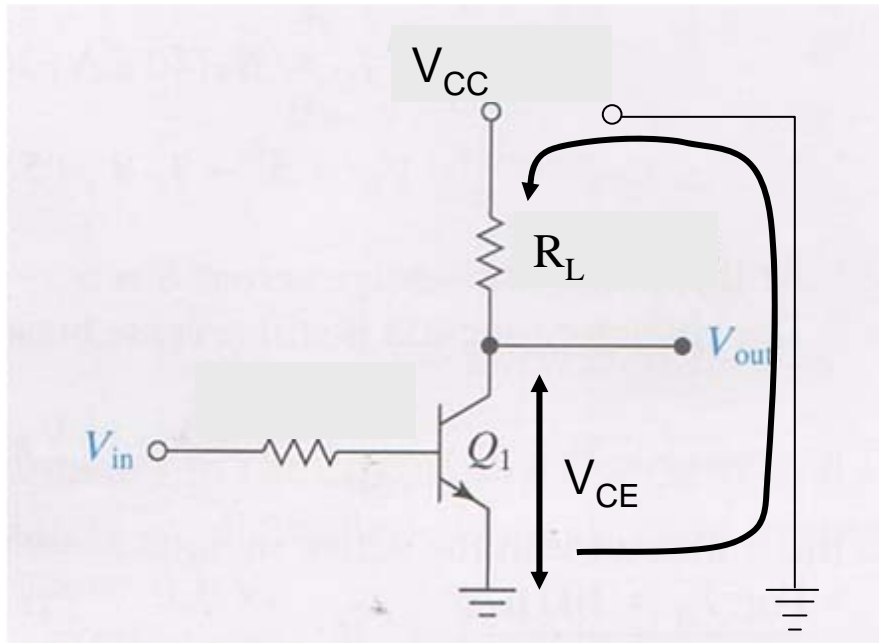BJT amplifier circuit analysis: Operating point



For an arbitrary collector voltage, collector current can be found using the KVL.

The KVL for the collector – emitter circuit, $V_{CC} = I_{RL} \times R_L + V_{CE}$;


$$I_{RL} = \frac{V_{CC} - V_{CE}}{R_L} \quad \text{The } R_L \text{ current depends linearly on the collector voltage } V_{CE}$$

Resistor R_L and the C-E circuit of BJT are connected in series, hence $I_{RL} = I_C$

For $I_b = 40 \mu\text{A}$ and $V_{CC} = 13\text{V}$, the collector current $I_C = 4 \text{ mA}$


For $I_b = 75 \mu\text{A}$ and $V_{CC} = 14\text{V}$, the collector current $I_C = 4 \text{ mA}$

BJT amplifier gain analysis: 1

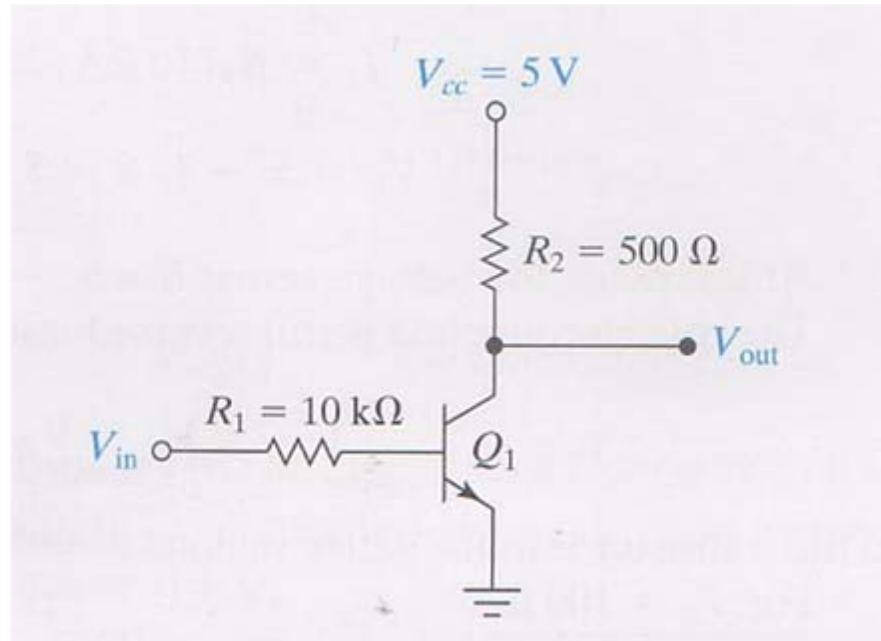


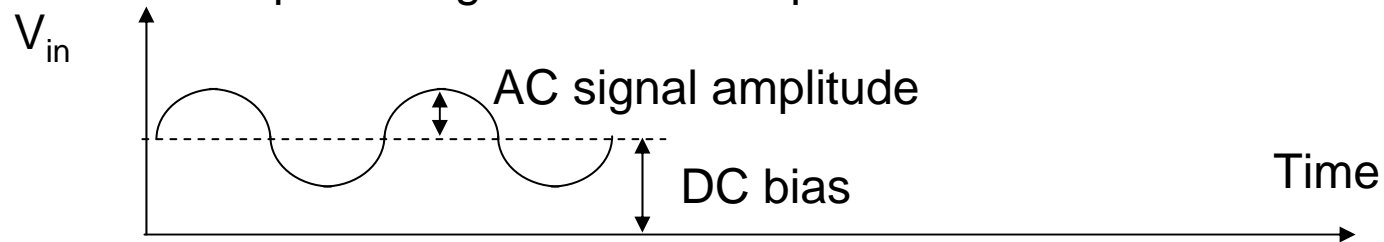
1. Input circuit

The input voltage has two components: the DC bias and the AC signal




DC voltage component biases the base-emitter p-n junction in the forward direction
AC component is the input signal to be amplified by the BJT.

BJT amplifier gain analysis: 2

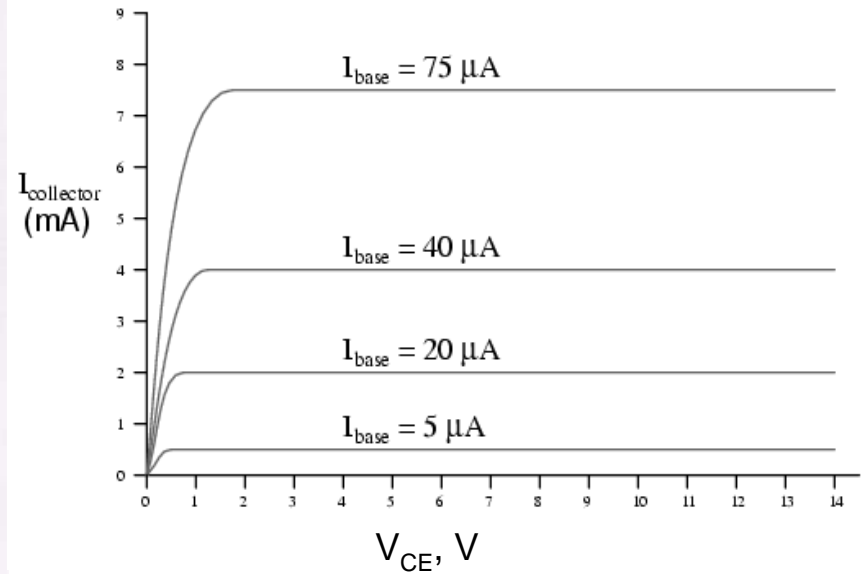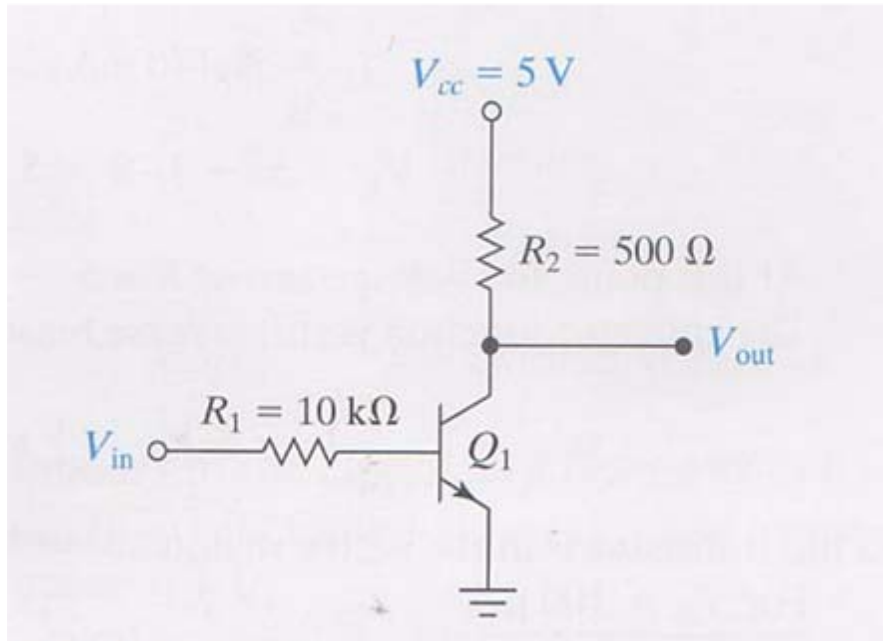


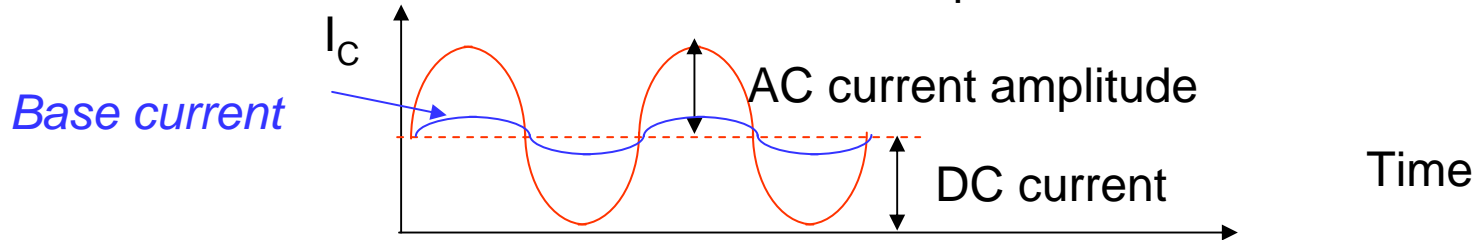
2. Output circuit

The collector current has two components too.



DC and AC collector currents flow through the BJT in accordance with its I-V characteristics

BJT amplifier gain analysis: 3

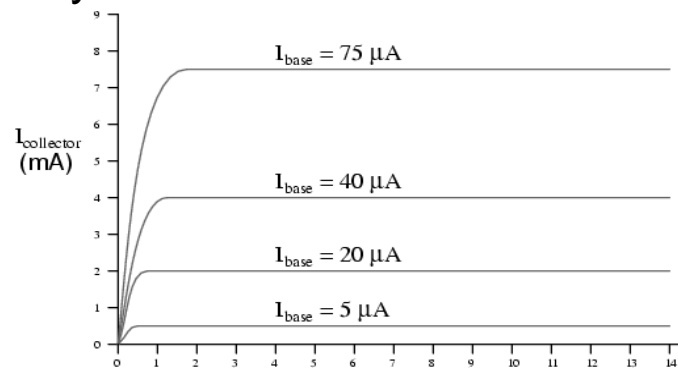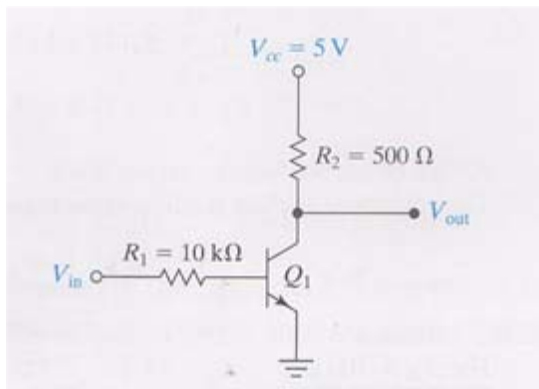

The resistance of the B-E junction is very low when $V_{BE} \geq V_{BE0} \approx V_{bi} \approx 0.7 \text{ V}$.

Hence the base current $I_B \cong (V_{in} - V_{BE0})/R_1 = (V_{inDC} - V_{BE0} + V_{inAC})/R_1$

The collector current I_C does not depend on the collector voltage if the latter is high enough.

Hence, $I_C \cong \beta I_B$;

The voltage drop across the load resistance R_2 : $V_2 = I_C R_2$;

The output voltage $V_{out} = V_{CC} - V_2 = V_{CC} - I_C R_2$;



$V_{out} = V_{CC} - I_C R_2 = V_{CC} - \beta I_B R_2 = V_{CC} - \beta R_2 (V_{inDC} - V_{BE0} + V_{inAC})/R_1$;

In signal amplifiers only AC component of the output voltage is important:

$$V_{outAC} = -\beta R_2 V_{inAC}/R_1;$$

The amplifier voltage gain: $k_V = V_{outAC}/V_{inAC} = -\beta R_2/R_1$;

BJT amplifier gain analysis: 4

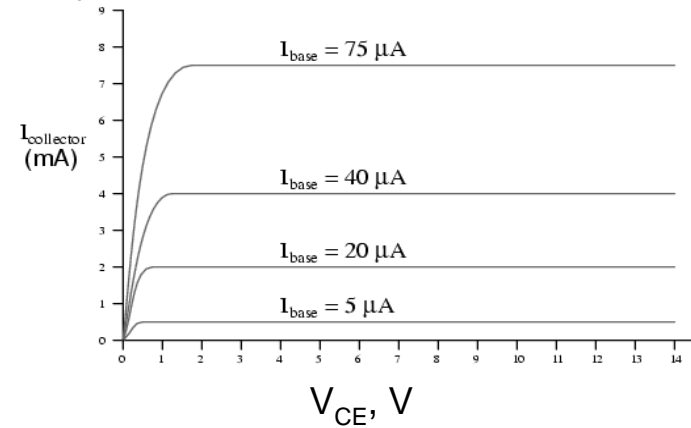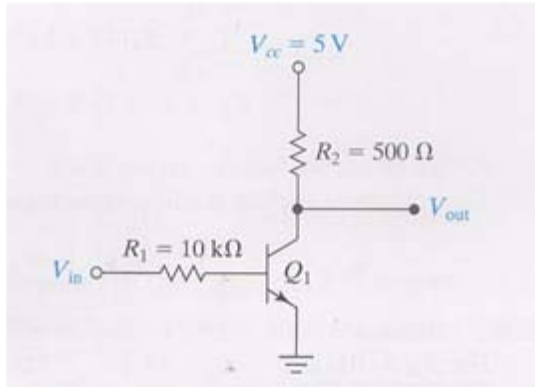


Common emitter gain summary:

Current gain: $k_I = \beta$


Voltage gain: $k_V = V_{outAC}/V_{inAC} = -\beta R_2/R_1$;

Power gain: $k_P = k_V \times k_I = -\beta^2 \times R_2/R_1$

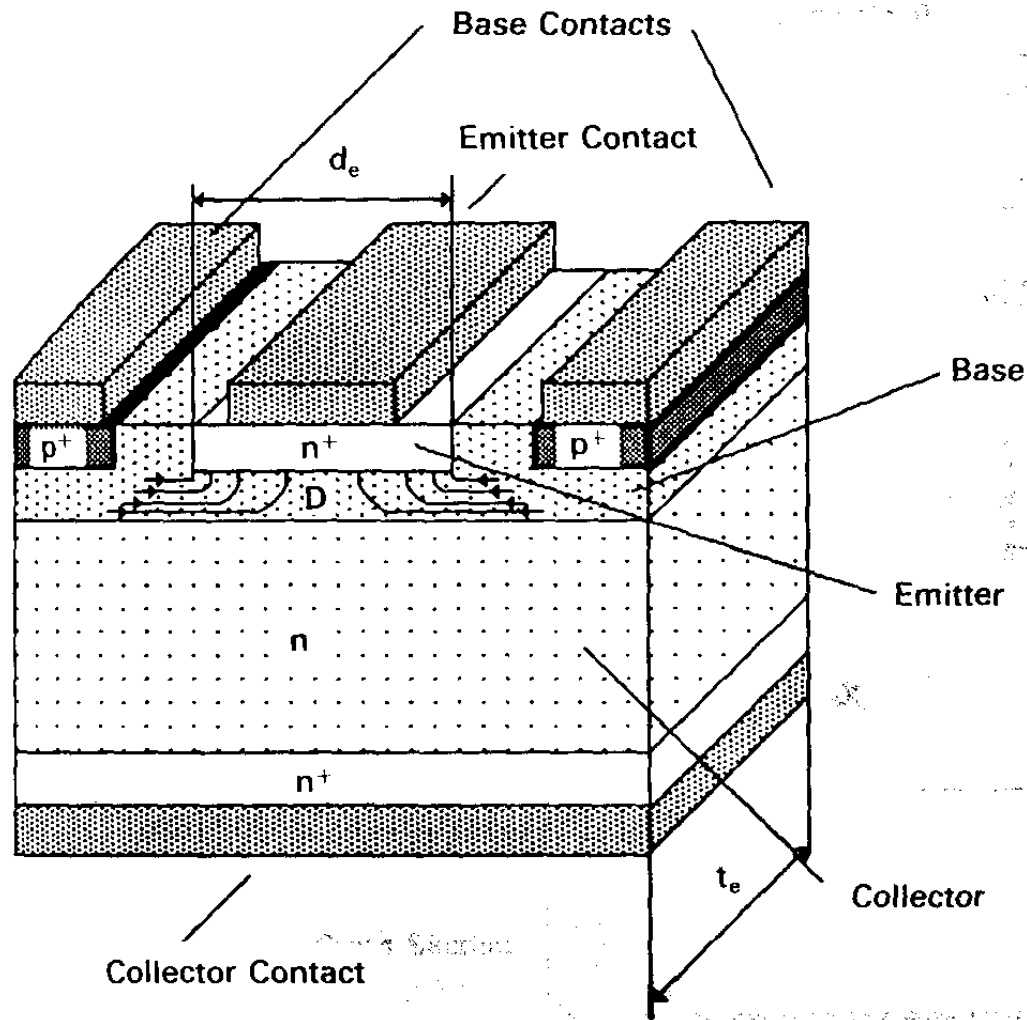BJT design and factors affecting the performance



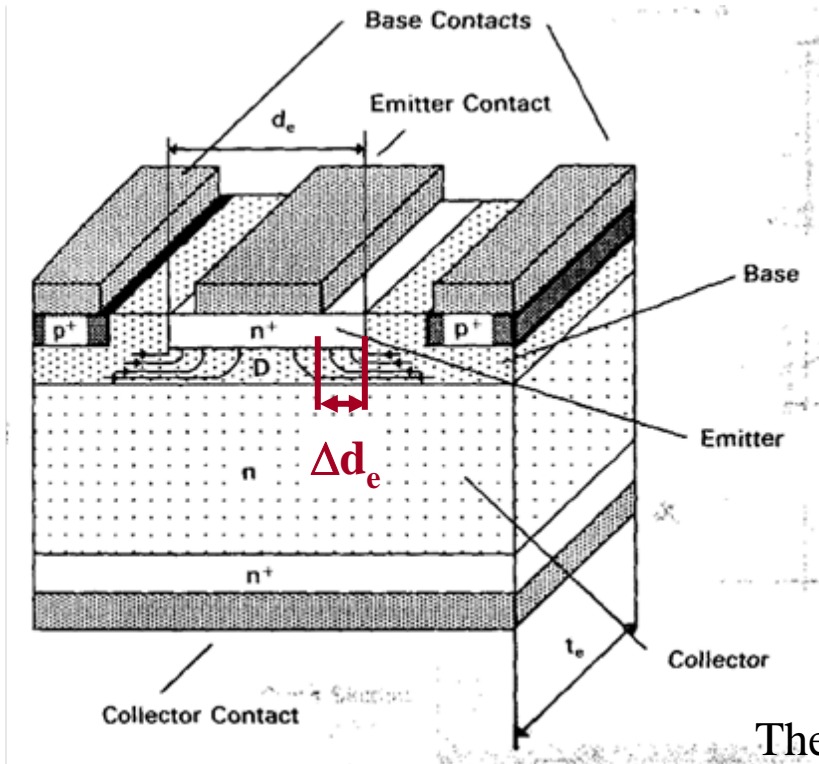Base resistance and emitter current crowding in BJTs



The voltage drop along the base layer $V_{bb} = r_{bb} I_b$, where r_{bb} is called the base spreading resistance.


The p-n junction current decreases rapidly when the voltage drops by $\Delta V_{bb} \sim V_{th} = kT/q$

$$I = I_S \left(e^{\frac{qV}{kT}} - 1 \right) = I_S \left(e^{\frac{V}{V_{TH}}} - 1 \right)$$

The length of the edge region, Δd_e , where most of the emitter current flows may be estimated from:

$$V_{th} = I_b R_{b_{max}} \approx I_b \rho_b \frac{\Delta d_e}{t_e W}$$

Emitter current crowding in BJTs (cont.)

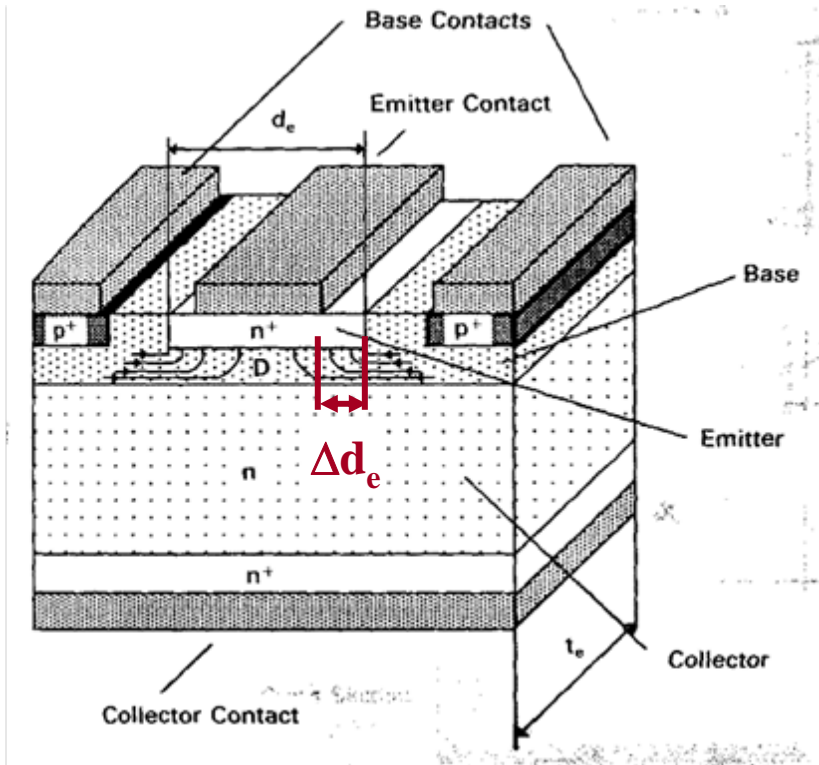


$$V_{th} = I_b R_{b\max} \approx I_b \rho_b \frac{\Delta d_e}{t_e W}$$

$$\rho_b = \frac{1}{q N_b \mu_b}$$

From these,

$$\Delta d_e \approx \frac{V_{th} t_e W}{I_b \rho_b} = \frac{V_{th}}{I_b} q N_b \mu_b t_e W_b$$

Example

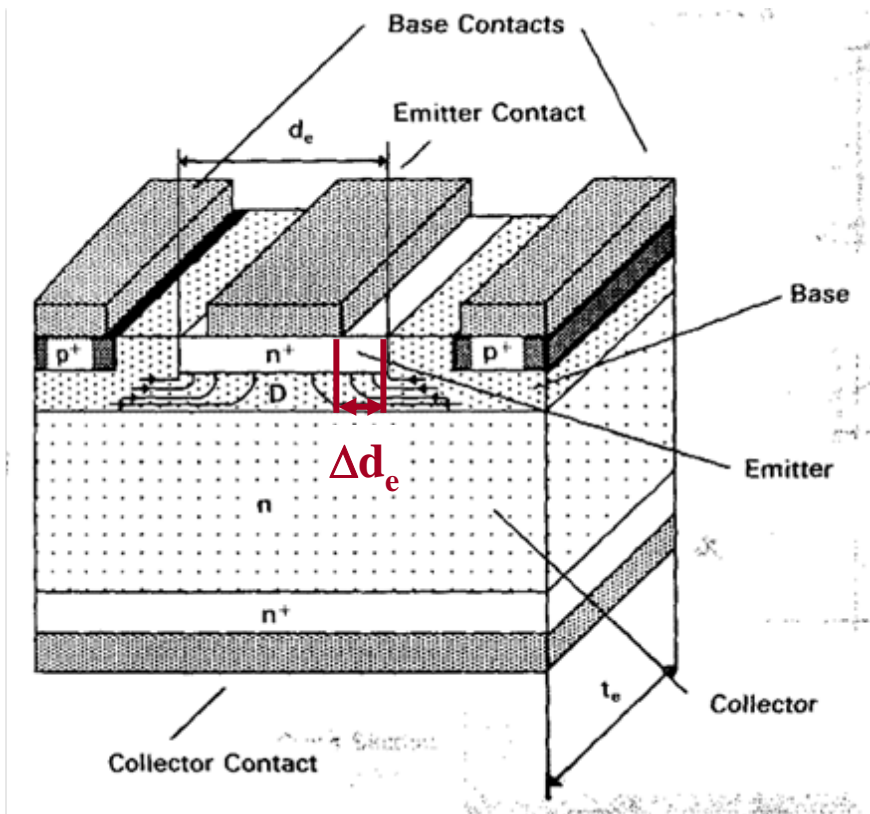

Estimate the effective emitter length, Δd_e for the BJT having the following parameters:

$$I_b = 50 \mu\text{A};$$

$$N_b = 10^{17} \text{ cm}^{-3}$$

$$\mu_b = 400 \text{ cm}^2/\text{V-s}$$



$$W_b = 0.1 \mu\text{m}$$

$$t_e = 100 \mu\text{m}$$

$$\Delta d_e \approx \frac{V_{th}}{I_b} q N_b \mu_b t_e W_b$$


$$\Delta d_e = 3.33 \text{ e-4 cm} = 3.33 \mu\text{m}$$

Large periphery BJT Design

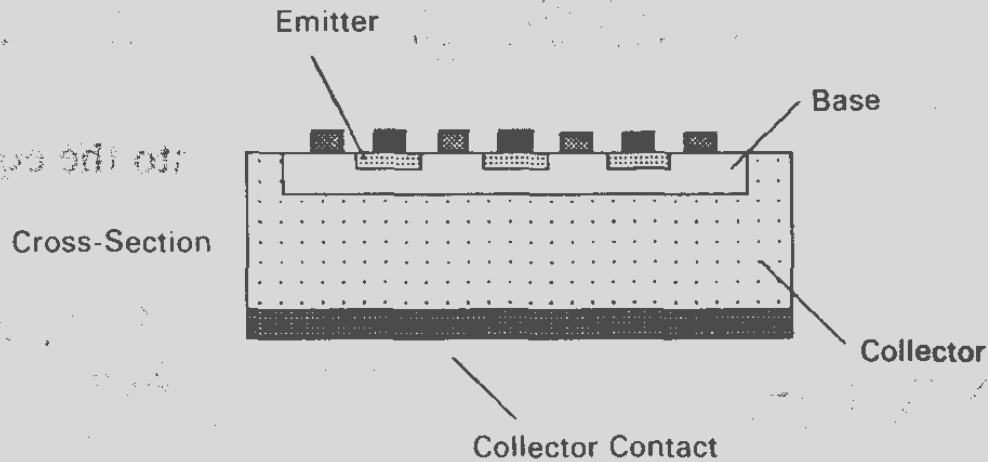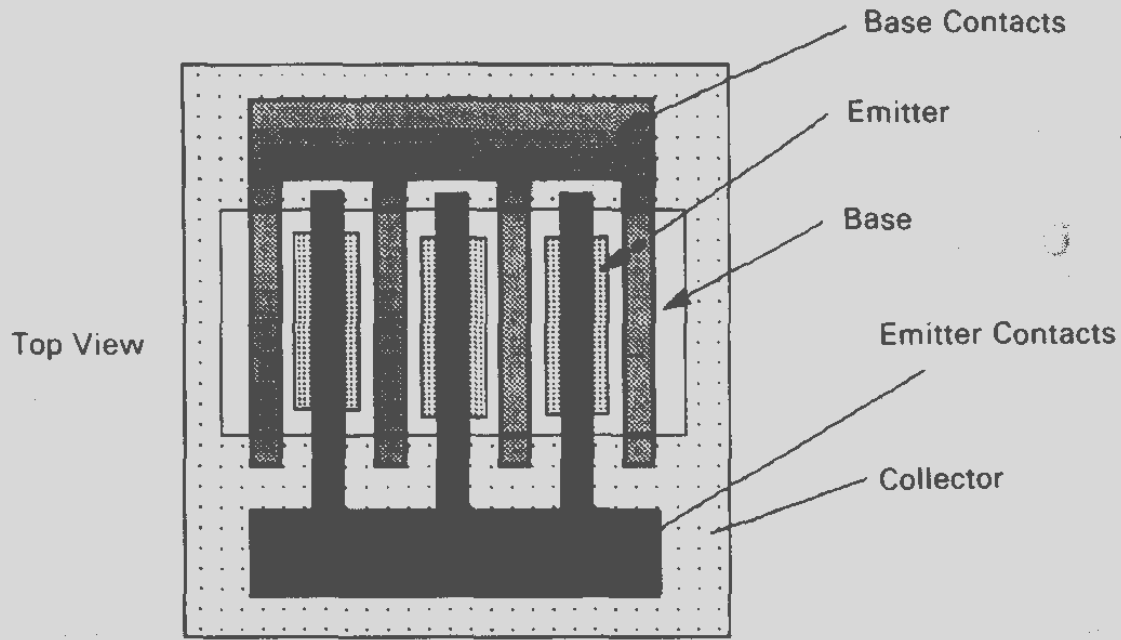

Base narrowing (Early effect)

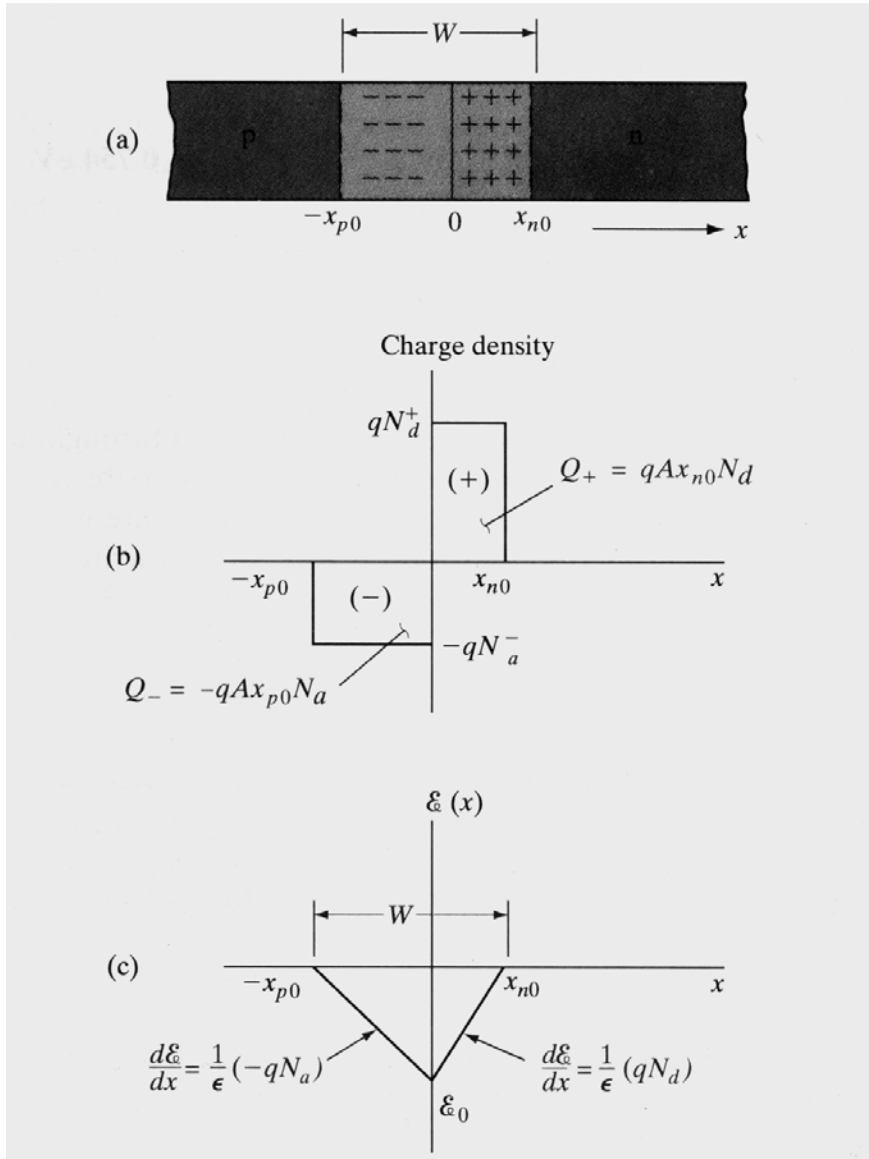The depletion width of the p-n junction depends on the applied voltage:



(Here W is the depletion region width not the width of the base as in BJT!)

In the BJT, this effect means that the effective width of the base is less than W_b :

$$W_{eff} = W_b - X_{deb} - X_{dcb}$$

where W_b is the physical thickness of the base,

x_{deb} and x_{dcb} are the depletion region widths from the emitter and collector sides.

The depletion widths are given by ($N_e \gg N_b$):

$$x_{deb} = \left[\frac{2\epsilon\epsilon_0 (V_{bi} - V_{be})}{q N_b} \right]^{1/2}$$

$$x_{dcb} = \left[\frac{2\epsilon\epsilon_0 (V_{bi} + V_{cb}) N_c}{q N_b^2} \right]^{1/2}$$

x_{dcb} is usually the most important factor since the voltage applied to collector is high.


The doping level in collector, N_{DC} has to be lower than that of the base, N_{AB} , to reduce the Early effect:

$$N_C \ll N_B$$

Due to Early effect the effective base thickness depends on the collector voltage.



In the gain expression, W should be replaced with W_{eff} :
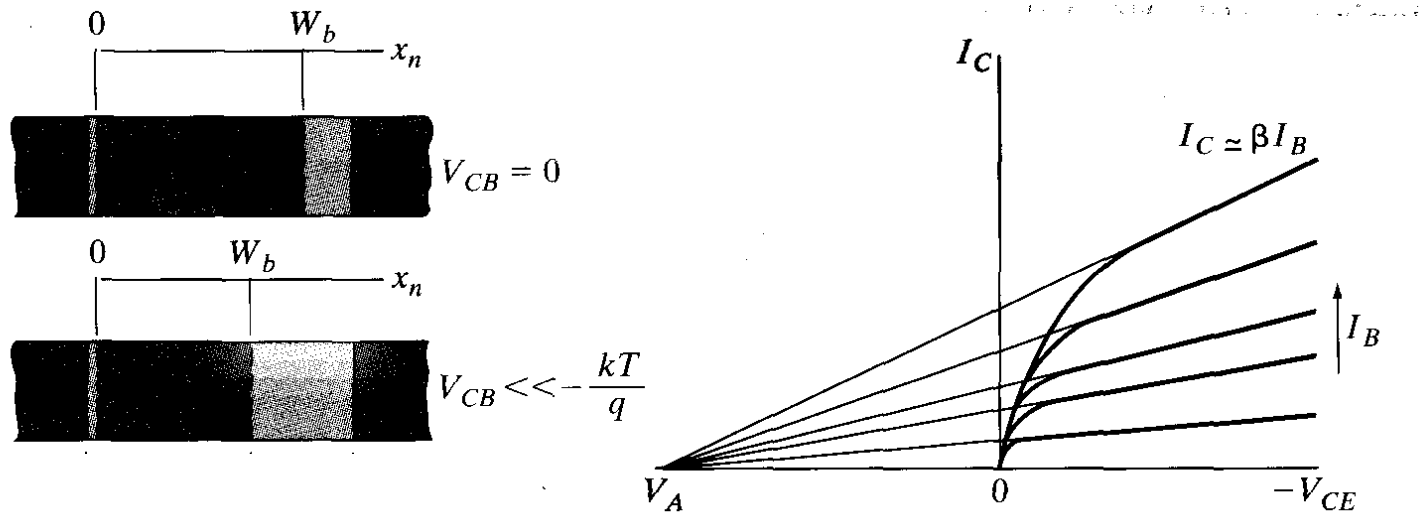
$$\beta_{\text{rec}} = \frac{2L_p^2}{W_{\text{eff}}^2}$$



The Early effect decreases the output resistance, and hence the voltage gain of BJTs.

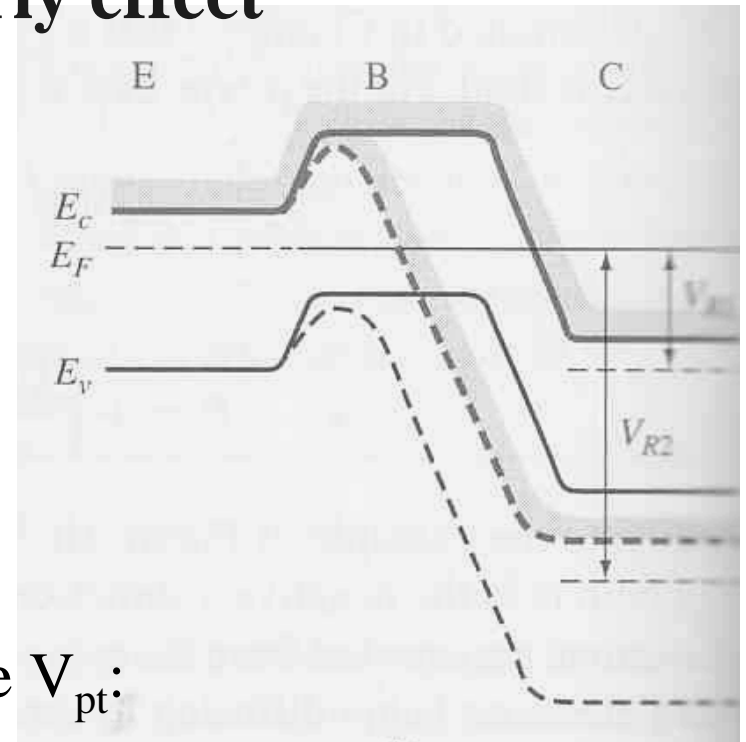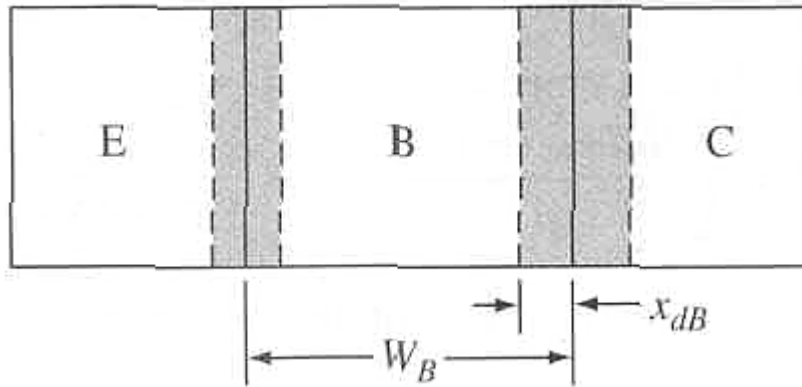Punch-through breakdown in BJTs - - the result of the Early effect




The punch-through breakdown voltage V_{pt} :

$$W = x_{dcb}$$

$$V_{pt} = \frac{qW^2}{2\epsilon\epsilon_0} \frac{N_b(N_c + N_b)}{N_c}$$

BJT Model

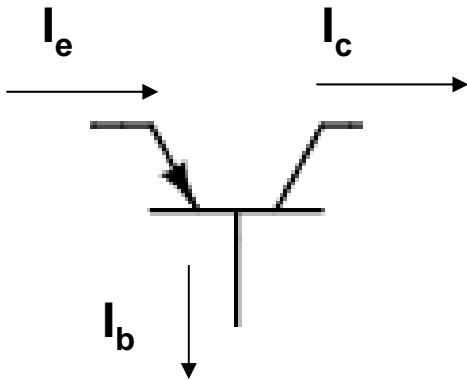- Gummel-Poon model used in SPICE and other simulators**



Applying KCL to the BJT terminals:

$$I_e = I_c + I_b$$

Collector – emitter current relationship:

$$I_c = \alpha I_e$$

where α is called a common base current gain

Hence,

$$I_c = \alpha (I_c + I_b)$$

$$I_c = \frac{\alpha}{1 - \alpha} I_b$$

$$I_c = \beta I_b$$


$$\beta = \frac{\alpha}{1 - \alpha}$$

$$\alpha = \frac{\beta}{1 + \beta}$$

Common emitter current gain is defined as:

The last two expressions link common emitter and common base current gains

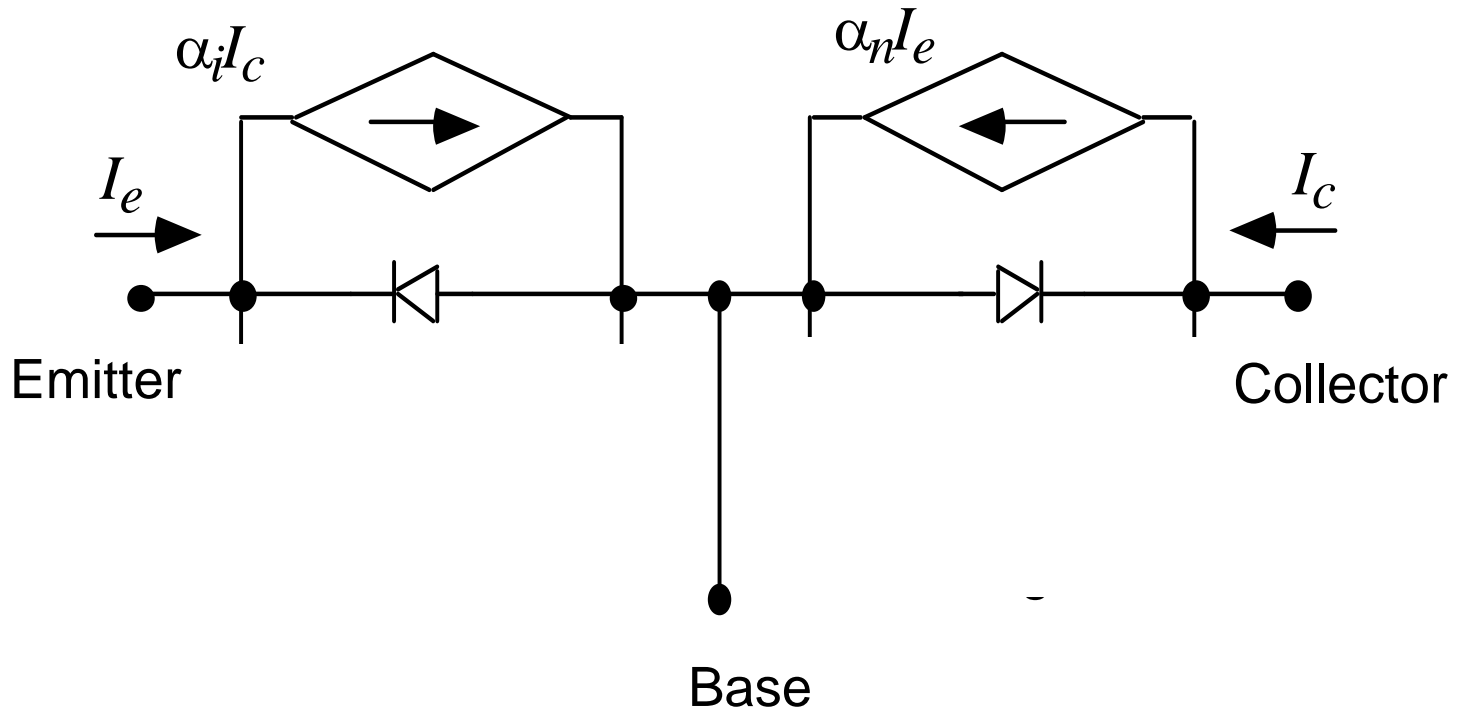Simplified Gummel-Poon BJT equivalent circuit



- Emitter junction:


$$I_{be} = \frac{I_{se}}{\beta_F} \left[\exp\left(\frac{V_{be}}{n_F V_{th}}\right) - 1 \right]$$

- Collector junction:

$$I_{bc} = \frac{I_{sc}}{\beta_R} \left[\exp\left(\frac{V_{bc}}{n_R V_{th}}\right) - 1 \right]$$

$$V_{th} = kT/q = 0.026 \text{ V at } 300 \text{ K}$$

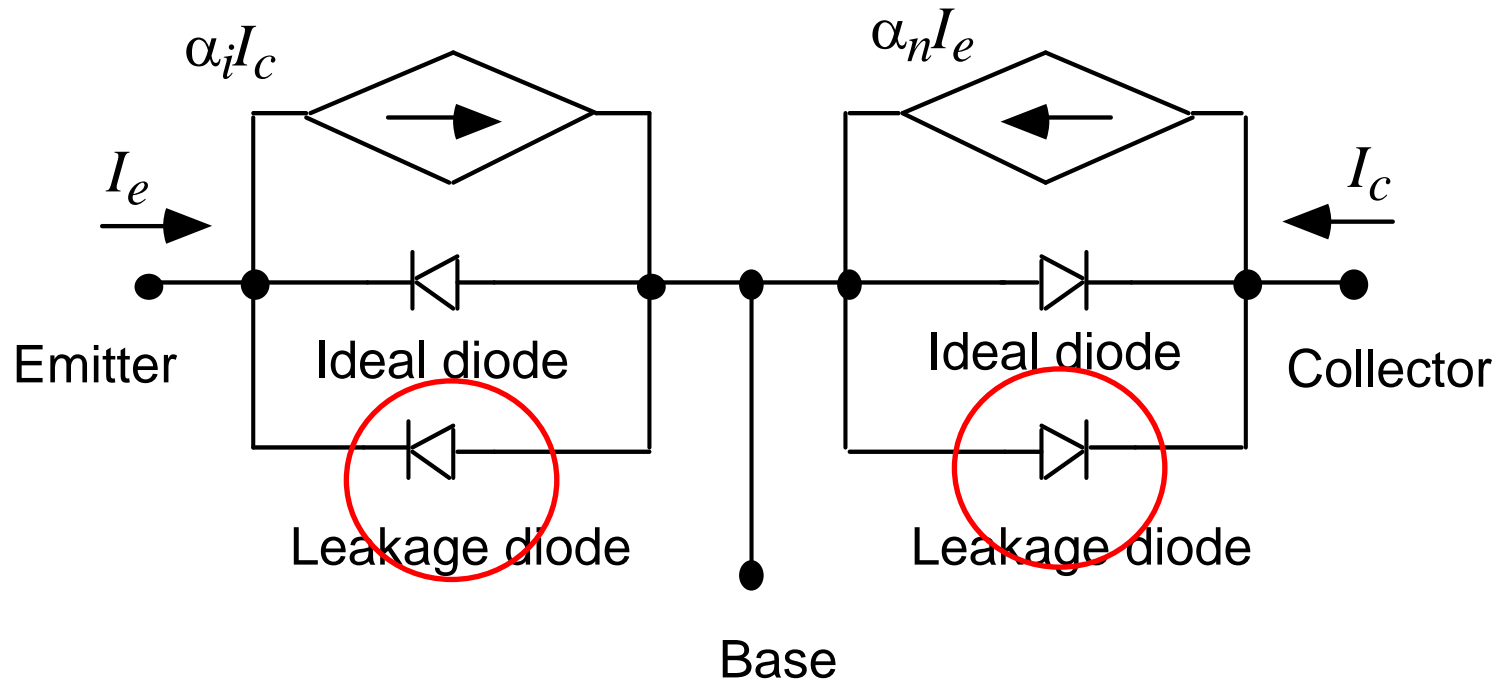Gummel-Poon BJT equivalent circuit accounting for the leakage currents



• Emitter –base leakage

diode:

$$I_{Leak_be} = I_{se} \left[\exp\left(\frac{V_{be}}{n_E V_{th}}\right) - 1 \right]$$

Collector –base leakage diode:

$$I_{Leak_bc} = I_{sc} \left[\exp\left(\frac{V_{bc}}{n_C V_{th}}\right) - 1 \right]$$